

## Week 1 Prelab

Briefly answer the following questions.

Name: Kevin Liu

1. Identify the resistors:

UID: 504862375



*Yellow-Violet-Orange-Gold*


47k  $\Omega$  with a tolerance of  $\pm$  5 %.



*Brown-Black-Yellow-Silver*

100k  $\Omega$  with a tolerance of  $\pm$  10 %.

2.

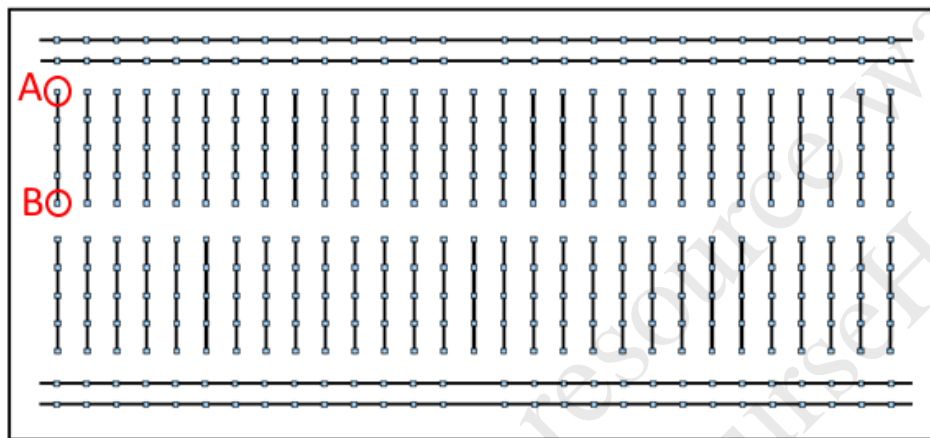


If a resistor is inserted into the breadboard with one leg at point A and one leg at point B, what resistance will an ohmmeter measure for that resistor? Why? What should you do instead to measure the proper resistance?


An ohmmeter will measure 0 because that row is already internally connected and current will bypass the resistor. To get the proper resistance, either leg A or leg B but not both should be moved to a connection on the column rows. Thereby only allowing current to travel through the resistor.

3. Draw the I-V curves for the following diagrams


(a) Ideal voltage source

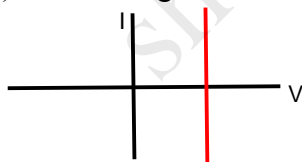


(c) Ideal current source

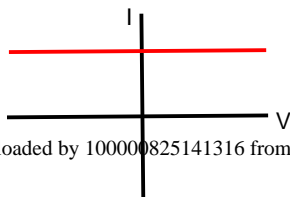

(b) Non-ideal voltage source

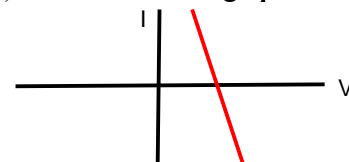


(d) Non-ideal current source

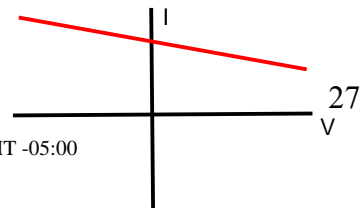

4. Prove the voltage and current divider equations: They are basic and very commonly used equations that you should memorize for use in all your future electronics courses.

### Voltage Divider

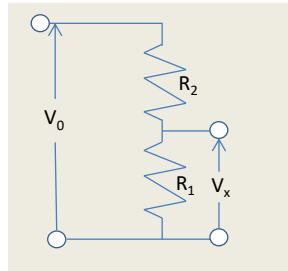

Problem: show that

$$V_x = V_0 R_1 / (R_1 + R_2)$$

YOUR SOLUTION HERE:

$$V_0 = I(R_1 + R_2)$$

$$I = V_0 / (R_1 + R_2)$$


$$V_x = I(R_1)$$

$$I = V_x / R_1$$

$$V_0 / (R_1 + R_2) = V_x / R_1$$

$$V_x = (V_0)(R_1) / (R_1 + R_2)$$

### Current Divider

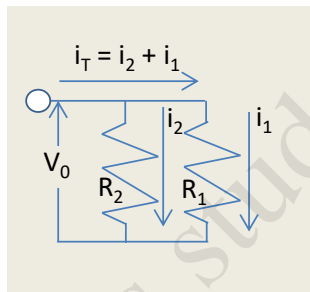

Problem: show that

$$I_1 = i_T R_2 / (R_1 + R_2)$$

YOUR SOLUTION HERE:

$$V_0 = i_T(R_{eq}) \quad R_{eq} = 1 / ((R_1 + R_2) / R_1 R_2) = R_1 R_2 / (R_1 + R_2)$$

$$V_0 = (I_1)(R_1)$$

$$V_0 = (i_T)(R_1)(R_2) / (R_1 + R_2)$$

$$(i_T)(R_1)(R_2) / (R_1 + R_2) = (I_1)(R_1)$$

$$I_1 = (i_T)(R_2) / (R_1 + R_2)$$

**Week 1 Prelab End**