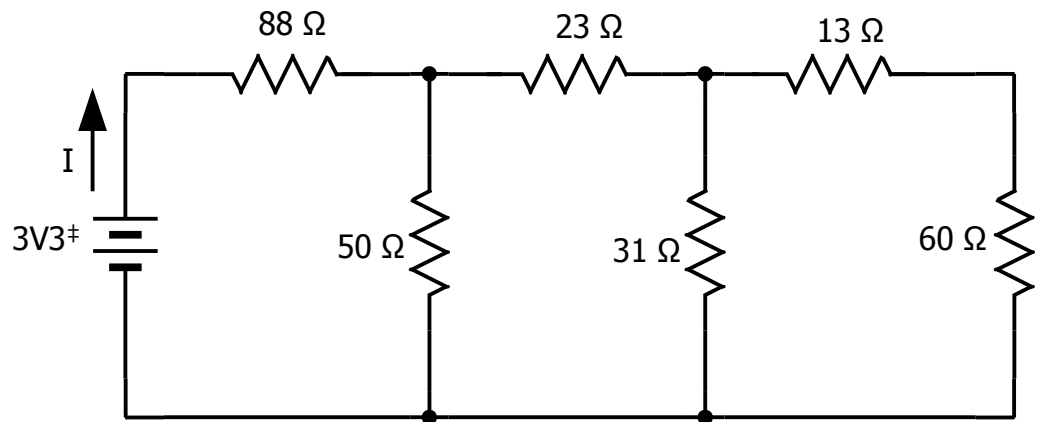


ECE3 Summer 2021

Practice Problems 1

1. Using your knowledge of series and parallel equivalents that you learned on p. 23 of the Week 1 lab, determine the current I .




$$I = 0.0296\text{ A} = 29.6\text{ mA}$$

[‡] 3V3 is shorthand for 3.3 V. You will see this often on schematics.

ECE3 Summer 2021


Practice Problems 1

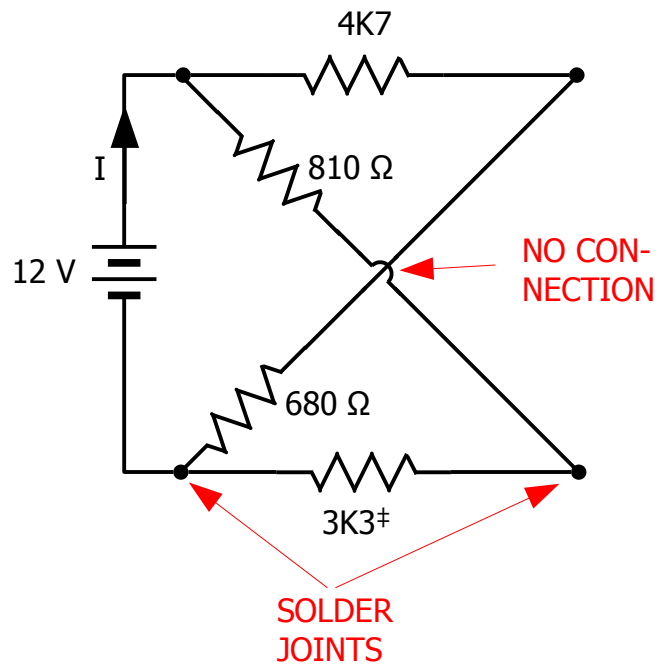2. Using your knowledge of series and parallel equivalents, determine the value of I .



$$I = 0.00515 \text{ A} = 5.15 \text{ mA}$$

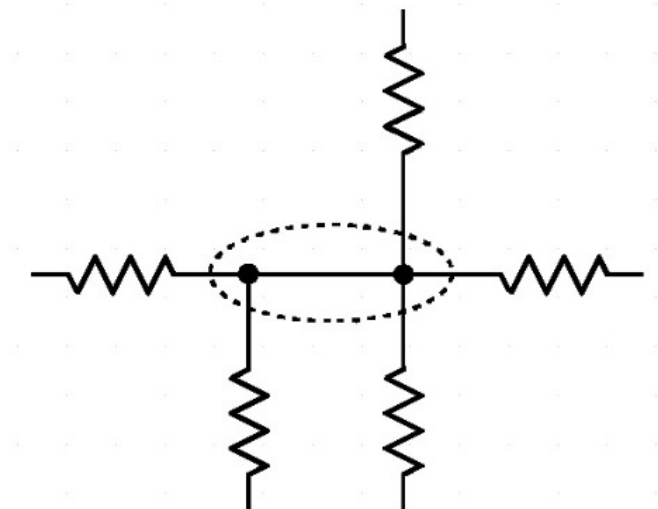3. This question may require a little digging on your part.



The circuit fragment inside the dotted ellipse is:


- Choose one answer.
- ☐ a. not a node
 - ☐ b. 1 node
 - ☐ c. 2 nodes

[‡] 3K3 is shorthand for 3.3K Ω . You will see this often on schematics.

ECE3 Summer 2021

Practice Problems 1

4.

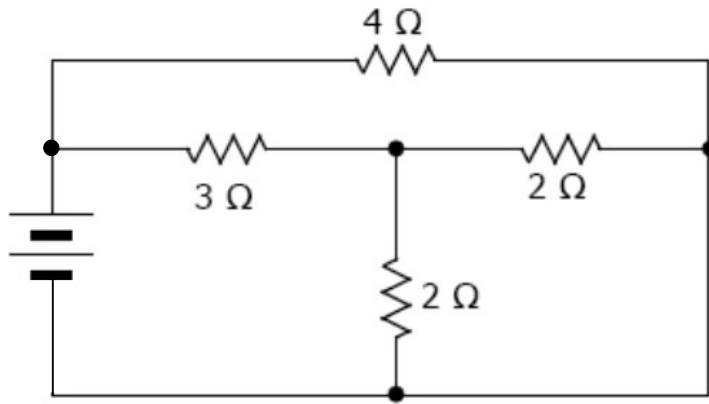

This circuit can be reduced to a voltage source and one resistor. What is the value of that one final resistor?

Challenge: try to do this one in your head: no paper/pencil, no calculator/computer. If you understand series and parallel, you can do it.

$2\ \Omega$




ECE3 Summer 2021

Practice Problems 1

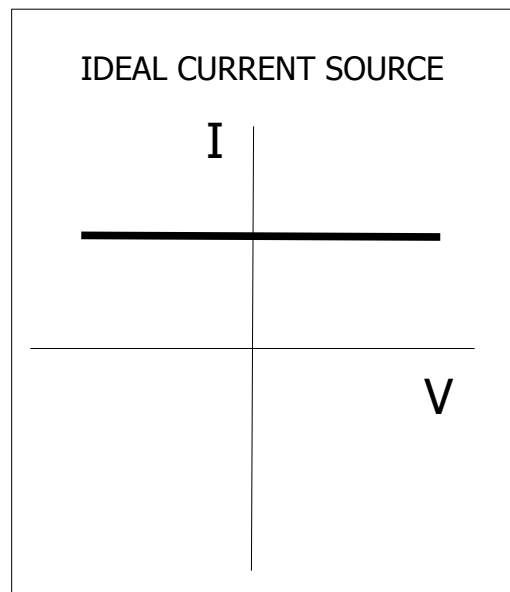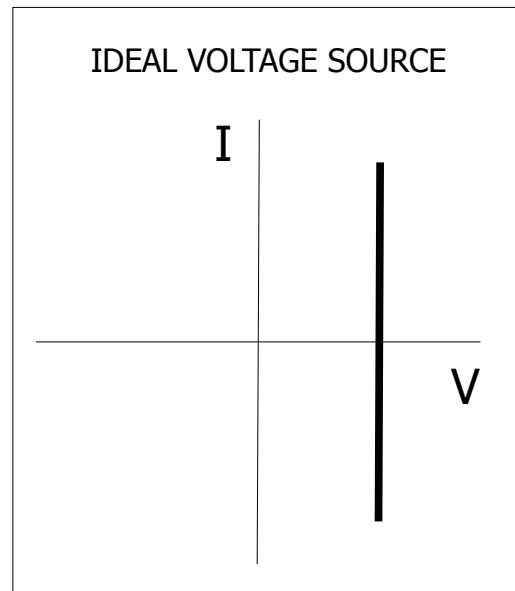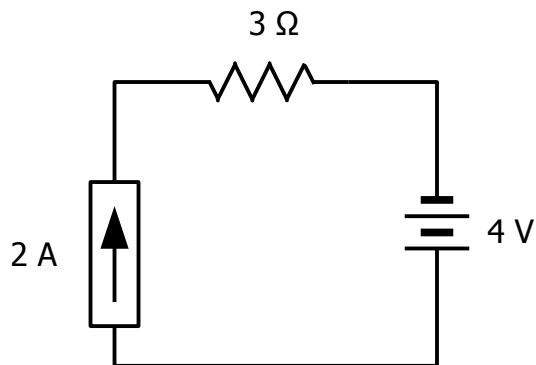5. Study the

[Khan Academy post on Passive Sign Convention.](#)


Then, using your knowledge of the I-V curves for voltage and current sources as explained in the YouTube videos, plus your knowledge of the Passive Sign Convention, determine if the 4 V battery is providing or absorbing power.



ECE3 Summer 2021

Practice Problems 1

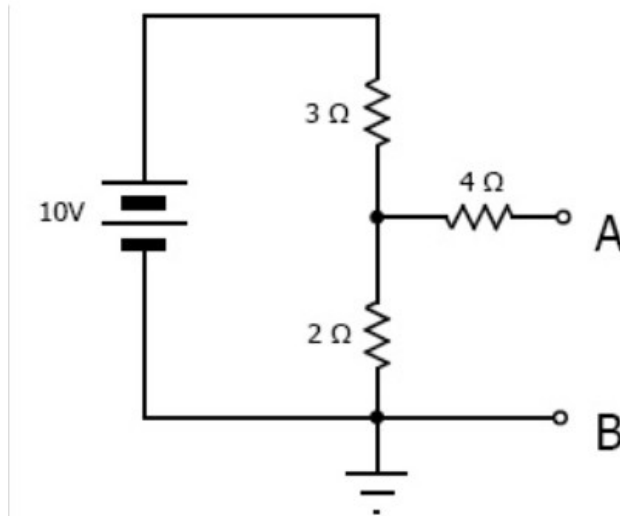
6. What is the voltage across the $4\ \Omega$ resistor? NOTE: you may consider this to be a trick question, but it has real meaning.



Choose
one
answer.

- ☐ a. 2.67 V
- ☐ b. 0.00 V
- ☐ c. 5.71 V
- ☐ d. 10.00 V
- ☐ e. 4.00 V

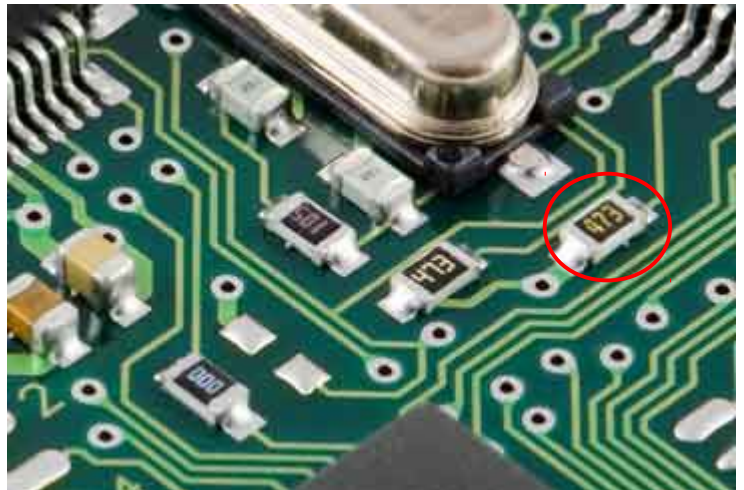
7. This is the picture of a surface mount resistor (labeled 473) on a PC board. Assuming that the three numbers correspond to the first three colors of a regular resistor, what is the resistance of this surface mount resistor?



ECE3 Summer 2021

Practice Problems 1

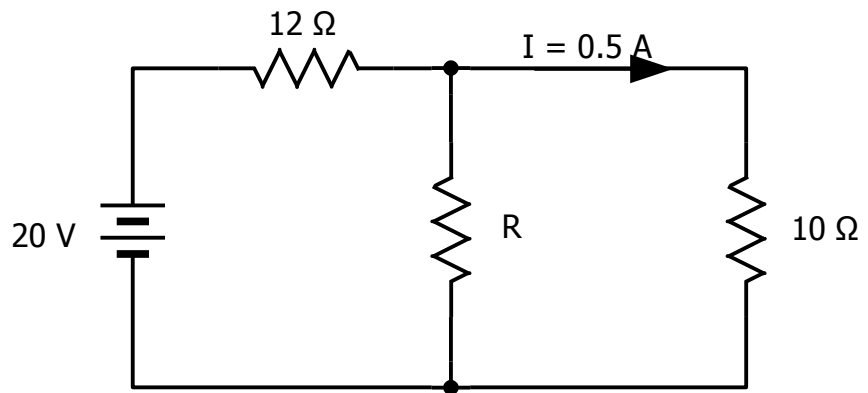8. Using your knowledge of series and parallel equivalents plus the Voltage Divider equation, determine the value of R .



$$R = 6.67 \, \Omega$$