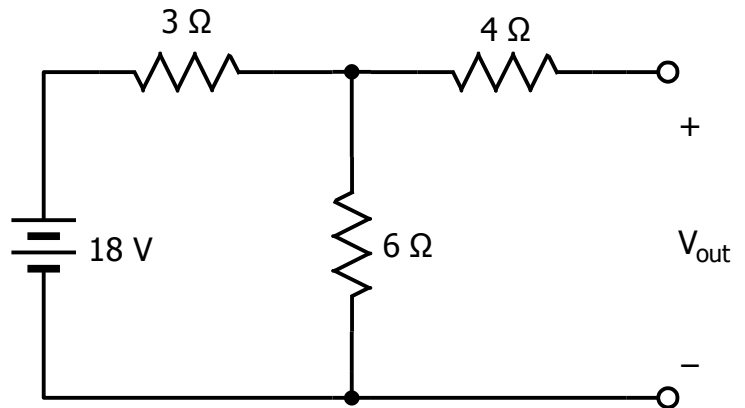


EE3 Fall 2021

Practice Problems 4

- Find the Thévenin equivalent circuit for the given circuit, using all three methods discussed in lecture.



$$V_{oc} = 18 \left(\frac{6}{6+3} \right) = 12 \text{ V}$$

R_{LOOK} Method:

$$R_{th} = 4 + 6 \parallel 3 = 6 \text{ } \Omega$$

$\frac{V_T}{I_T}$ Method:

$$I_T = \frac{V_T}{4 + 3 \parallel 6}$$

$$R_{th} = \frac{V_T}{I_T} = 6 \text{ } \Omega$$

$\frac{V_{oc}}{I_{sc}}$ Method:



$$\frac{V_1 - 18}{3} + \frac{V_1}{6} + \frac{V_1}{4} = 0$$

$$9V_1 - 72 = 0$$

$$V_1 = 8 \text{ V}$$

$$I_{sc} = \frac{V_1}{4} = 2 \text{ A}$$
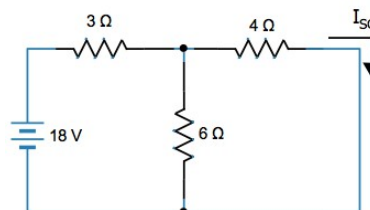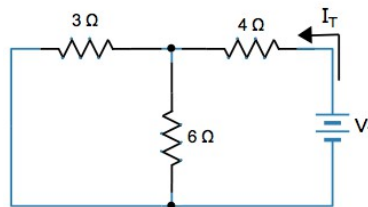
$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{12}{2} = 6 \text{ } \Omega$$




EE3 Fall 2021

Practice Problems 4

2a. Use Node Voltage Analysis to find V_{OC} .

Hint: find an expression for I_2 .

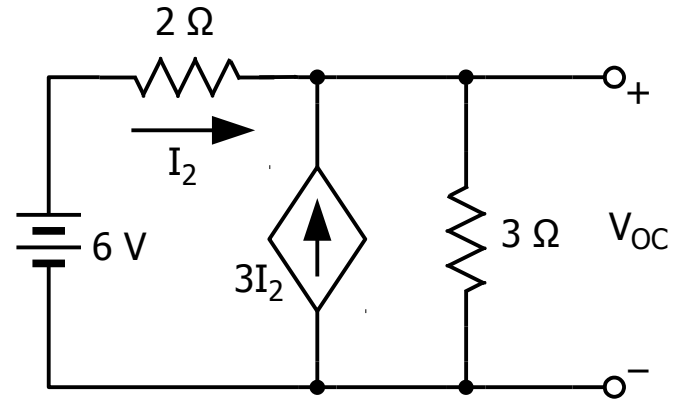2b. Use both allowable methods to find R_{th} .



$$\frac{V_{OC}-6}{2} - 3I_2 + \frac{V_{OC}}{3} = 0$$

$$I_2 = \frac{6-V_{OC}}{2}$$

$$\frac{V_{OC}-6}{2} - \frac{18-3V_{OC}}{2} + \frac{V_{OC}}{3} = 0$$

$$3V_{OC} - 18 - 54 + 9V_{OC} + 2V_{OC} = 0$$

$$V_{OC} = 5.14 \text{ V}$$


$\frac{V_T}{I_T}$ Method:

$$\frac{V_T}{2} + \frac{V_T}{3} - 3I_2 - I_T = 0$$

$$I_2 = \frac{0-V_T}{2}$$

$$\frac{5V_T}{6} + \frac{3V_T}{2} = I_T = V_T \left(\frac{14}{6} \right)$$
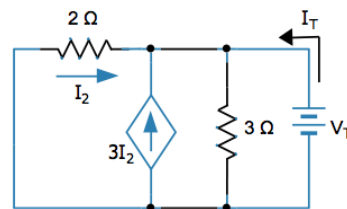
$$R_{th} = \frac{V_T}{I_T} = 0.43 \Omega$$



$\frac{V_{OC}}{I_{SC}}$ Method:


$$\frac{0-6}{2} - 3I_2 + \frac{0}{3} + I_{SC} = 0$$

$$I_2 = \frac{6-0}{2} = 3$$

$$-3 - 3(3) + 0 = -I_{SC}$$

$$I_{SC} = 12 \text{ A}$$
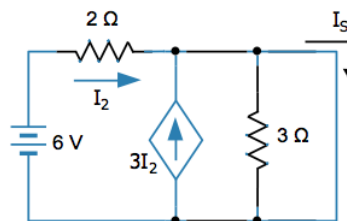
$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{5.14}{12} = 0.43 \Omega$$




EE3 Fall 2021

Practice Problems 4

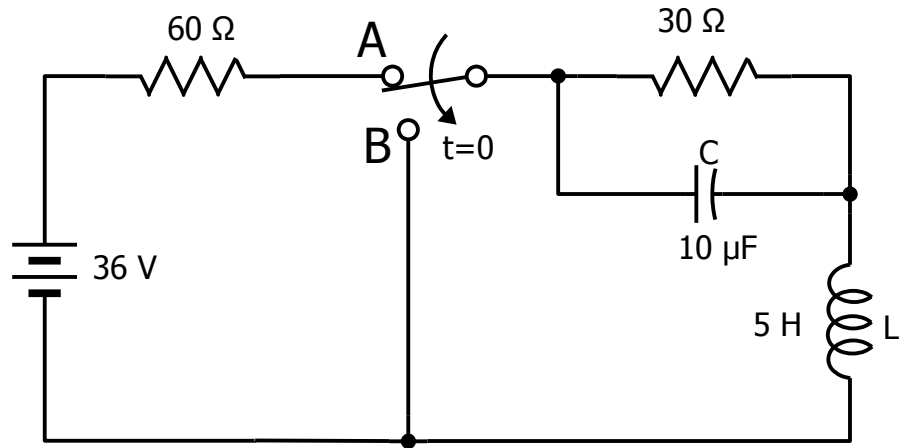3. The switch has been in position A for a LONG TIME before switching to position B at $t = 0$.

- Find magnitude & direction of $i_L(0^-)$
- Find magnitude and polarity of $v_C(0^-)$
- Find magnitude and polarity of $v_L(0^+)$
- Find magnitude and direction of $i_R(0^+)$
- Find magnitude and direction of $i_C(0^+)$



$$i_L(0^-) = \frac{36}{60+30} = 0.4 \text{ A (down)}$$

$$v_C(0^-) = (0.4)(30) = 12 \text{ V (plus to left)}$$

$$v_L(0^+) = v_C(0^+) = v_C(0^-) = 12 \text{ V (+ to bottom)}$$

$$i_R(0^+) = \frac{12 \text{ V}}{30 \Omega} = 0.4 \text{ A (left to right)}$$

Currents at top of inductor:

$$i_L(0^+) = +0.4 \text{ A}$$

$$i_R(0^+) = -0.4 \text{ A}$$


$$\text{By KCL, } i_C(0^+) + 0.4 - 0.4 = 0$$

$$\therefore i_C(0^+) = 0$$

EE3 Fall 2021

Practice Problems 4

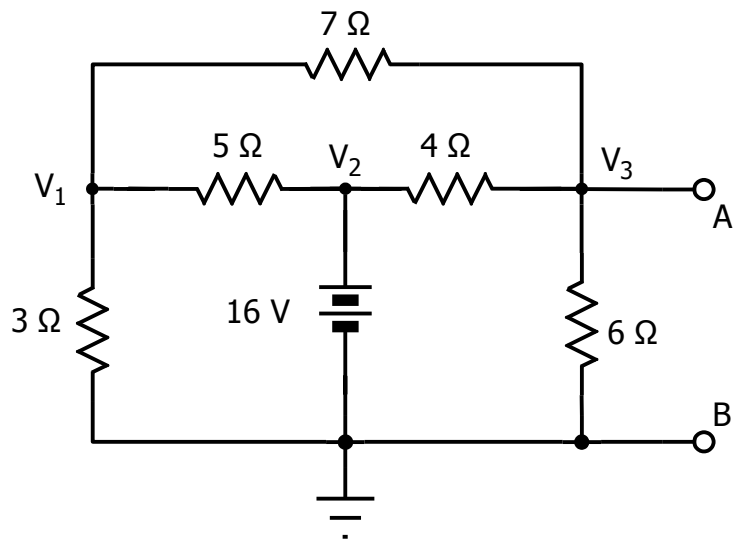- 4.
- Given the $V_3 = 8.8 \text{ V}$, use the V_{OC} - I_{SC} method to find the Thévenin Equivalent circuit, looking in through Port A-B.
 - Compare your R_{th} to the answer in Problem 5.



From Practice Problems 3, $V_3 = 8.8 \text{ V}$

$$V_{OC} = V_3 = 8.8 \text{ V}$$

Shorting Terminals A and B,

$$\frac{V_1 - 16}{5} + \frac{V_1}{3} + \frac{V_1}{7} = 0$$

$$\frac{0 - 16}{4} + \frac{0 - V_1}{7} + I_{SC} = 0$$

$$V_1 = \frac{336}{71} = 4.7324$$

$$I_{SC} = \frac{V_1 + 112}{28} = 4.6761$$


$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{8.8}{4.6761} = 1.88 \text{ } \Omega$$

NOTE: This problem shows Method (a.) to finding the Thévenin Equivalent circuit.

EE3 Fall 2021

Practice Problems 4

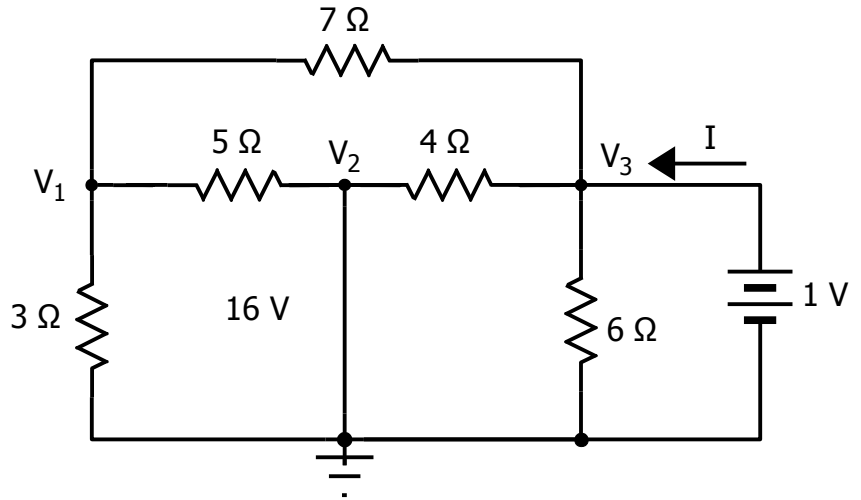5. This is the circuit that we studied in Problem 4. This time, you will find the Thévenin Equivalent circuit by using Method (b.). V_{oc} does not change. For R_{th} , we replaced the 16 V battery with a short and attached a 1 V battery to the circuit as shown.
- Find the current I .
 - Compute $1 \text{ V} / I$. Units are ohms.
 - Compare your answer to Problem 4.



$$V_2 = 0 \text{ V}; V_3 = 1 \text{ V}$$

$$\frac{V_1 - 0}{3} + \frac{V_1 - 0}{5} + \frac{V_1 - 1}{7} = 0$$

$$V_1 = \frac{15}{71} = 0.2113 \text{ V}$$

$$-I + \frac{1 - 0 \text{ V}}{4 \Omega} + \frac{1 \text{ V}}{6 \Omega} + \frac{1 - 0.2113 \text{ V}}{7 \Omega} = 0$$


$$I = 0.53 \text{ A}$$

$$R_{th} = \frac{1 \text{ V}}{I} = \frac{1}{0.53} = 1.89 \Omega$$

EE3 Fall 2021

Practice Problems 4

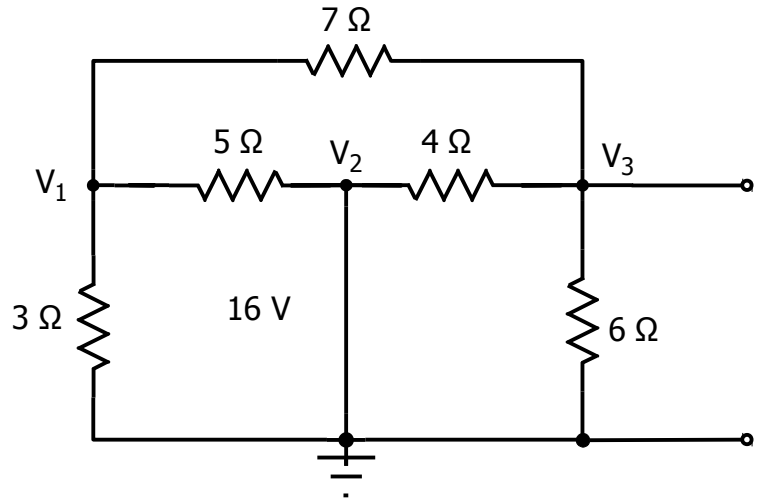6. This is the circuit that we studied in Problem 1. This time, you will find the Thévenin Equivalent circuit by using Method (c.). We replaced the 16 V battery with a short.
- Using your knowledge of series and parallel circuits, find the resistance of the circuit when looking in through the port.
 - Compare your answer to Problem 4.




$$R_{th} = (7+5||3) || (4||6) = 1.89 \, \Omega$$

EE3 Fall 2021

Practice Problems 4

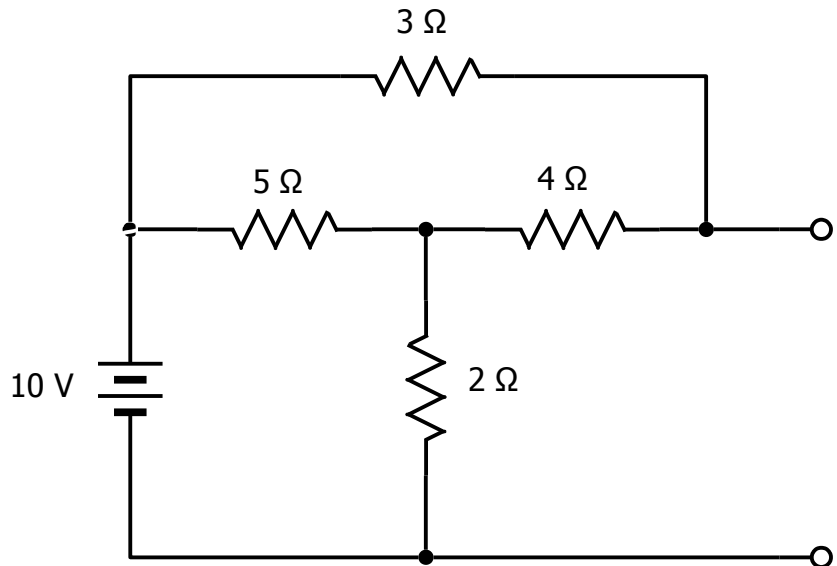7. Find the Thévenin Equivalent circuit, using Method a.



Finding V_{OC} : let V_1 be the voltage at the top of the 2Ω resistor.

$$\frac{V_1 - 10}{5} + \frac{V_1}{2} + \frac{V_1 - V_{OC}}{4} = 0$$

$$\frac{V_{OC} - 10}{3} + \frac{V_{OC} - V_1}{4} = 0$$

$$4V_1 + 10V_1 + 5V_1 - 5V_{OC} = 40$$

$$-3V_1 + 3V_{OC} + 4V_{OC} = 40$$

$$V_{OC} = 7.46 \text{ V}$$

Finding I_{SC} :

$$\frac{V_1 - 10}{5} + \frac{V_1}{2} + \frac{V_1}{4} = 0$$

$$\frac{0 - 10}{3} + \frac{0 - V_1}{4} + I_{SC} = 0$$

$$4V_1 + 10V_1 + 5V_1 = 40$$

$$-3V_1 + 12I_{SC} = 40$$

$$I_{SC} = 3.86 \text{ A}$$

$$R_{th} = \frac{V_{OC}}{I_{SC}} = 1.93 \Omega$$

EE3 Fall 2021

Practice Problems 4

8. Find the Thévenin
Equivalent circuit, using
Method c.

