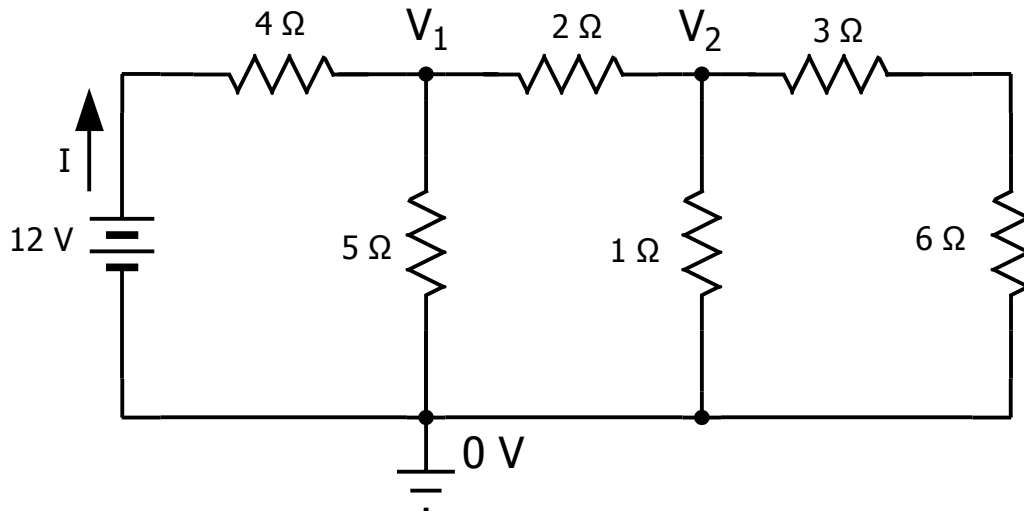


EE3 Fall 2021

Practice Problems 2



- This is a similar circuit to that in Lecture1. Only the resistor values are different. It can be solved using series-parallel equivalents. But solve it using the NVA process below.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the $4\ \Omega$ resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the $5\ \Omega$ resistor.
 - Continuing, write an expression for the current through the $2\ \Omega$ resistor.
 - Now, following the same procedure, write Ohm's Law expressions for the three currents leaving Node 2.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Combine the three answers to 1d into a KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

Currents leaving a node are given + signs. By the Passive Sign Convention, the end of the resistor where the current enters must be the + end.

$$1a. \frac{V_1 - 12}{4}$$

$$1b. \frac{V_1 - 0}{5}$$

$$1c. \frac{V_1 - V_2}{2}$$

$$1d. \frac{V_2 - V_1}{2}; \frac{V_2 - 0}{1}; \frac{V_2 - 0}{3+6}$$

$$1e. \frac{V_1 - 12}{4} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0$$

$$1f. \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{1} + \frac{V_2 - 0}{3+6} = 0$$

$$2. \text{ From 1e: } 19V_1 - 10V_2 = 60$$

$$\text{ From 1f: } -9V_1 + 29V_2 = 0$$


$$V_1 = 3.7744\text{ V}; V_2 = 1.1714\text{ V}$$

$$3. I = \frac{12 - 3.77}{4} = 2.06\text{ A}$$

EE3 Fall 2021 Practice Problems 2

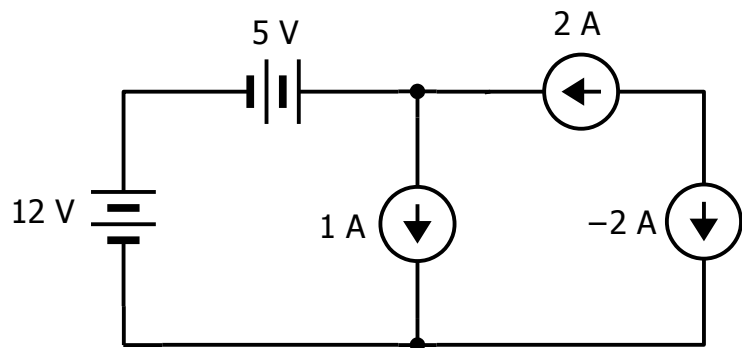
4. Is this a "legal" circuit? If not, why not?

Circuit is legal.
KVL is satisfied in all three loops.
KCL is satisfied at both nodes.



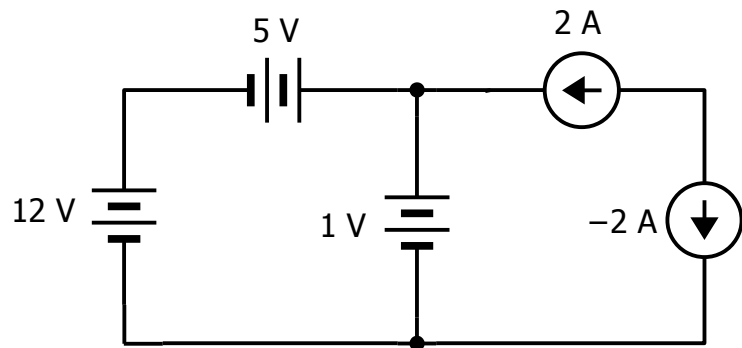5. Is this a "legal" circuit? If not, why not?

Circuit is illegal.
KVL not satisfied in left loop.




EE3 Fall 2021

Practice Problems 2

6. Using your knowledge of Node Voltage Analysis (NVA), find the current I .

$$I = 2.24 \text{ A}$$

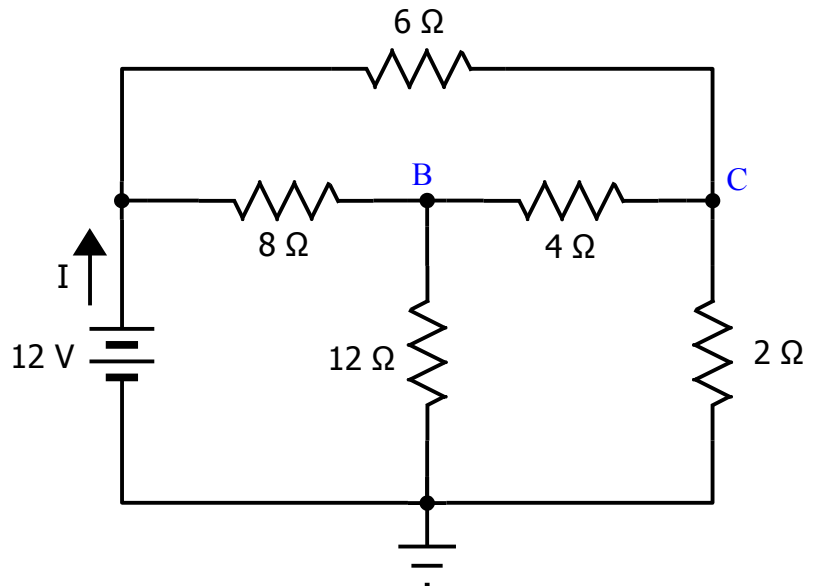

$$\text{Node B: } \frac{V_B - 12}{8} + \frac{V_B}{12} + \frac{V_B - V_C}{4} = 0$$

$$\text{Node C: } \frac{V_C - V_B}{4} + \frac{V_C}{2} + \frac{V_C - 12}{6} = 0$$

$$\text{Node B: } \left(\frac{1}{8} + \frac{1}{12} + \frac{1}{4} \right) V_B - \left(\frac{1}{4} \right) V_C = \left(\frac{1}{8} \right) 12$$

$$\text{Node C: } \left(\frac{-1}{4} \right) V_B + \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{6} \right) V_C = \left(\frac{1}{6} \right) 12$$

2x2 matrix to get V_B and V_C .


$$V_B = 5.243 \text{ V}; V_C = 3.612 \text{ V.}$$

$$\text{KCL at top of battery: } -I + \frac{12 - V_B}{8} + \frac{12 - V_C}{6} = 0$$

$$I = 2.24 \text{ A}$$

EE3 Fall 2021 Practice Problems 2

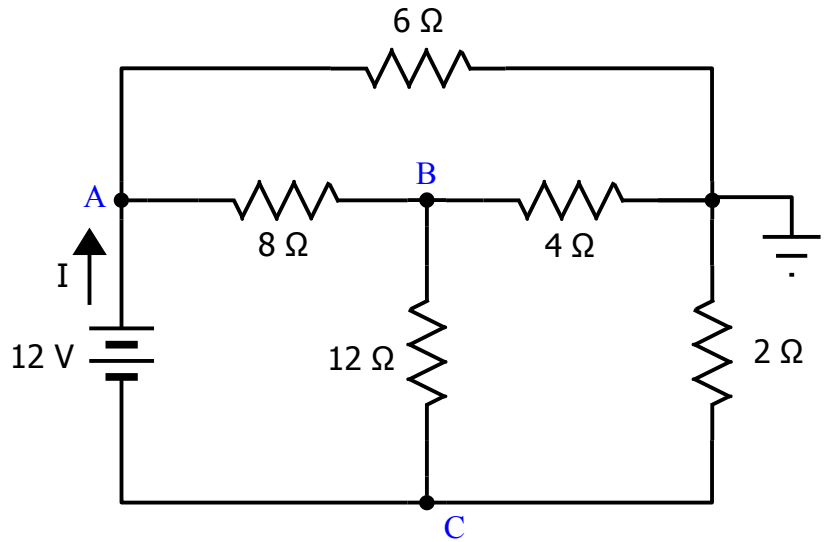7. This is the same circuit as Problem 6. Using your knowledge of Node Voltage Analysis (NVA), find the current I . HINT: Use I as an unknown fourth variable. (Note: with the reference node at a different location, you now have 3 unknown nodes. But you also know the voltage relationship between 2 of them.)



$$I = 2.24 \text{ A}$$

$$\text{Node A: } -I + \frac{V_A - V_B}{8} + \frac{V_A - 0}{6} = 0$$

$$\text{Node B: } \frac{V_B - V_A}{8} + \frac{V_B - V_C}{12} + \frac{V_B - 0}{4} = 0$$

$$\text{Node C: } +I + \frac{V_C - V_B}{12} + \frac{V_C - 0}{2} = 0$$

$$V_A = V_C + 12$$

$$-24I + 7V_A - 3V_B + 0V_C = 0$$

$$0I - 3V_A + 11V_B - 2V_C = 0$$

$$12I + 0V_A - V_B + 7V_C = 0$$


$$0I + V_A + 0V_B - V_C = 12$$

$$I = 2.24 \text{ A}; V_A = 8.39 \text{ V}; V_B = 1.63 \text{ V}; V_C = -3.61 \text{ V}$$

Note that $V_B - V_C = 5.24 \text{ V}$ (compare to V_B in Problem 6). Try the other equivalencies.

EE3 Fall 2021 Practice Problems 2

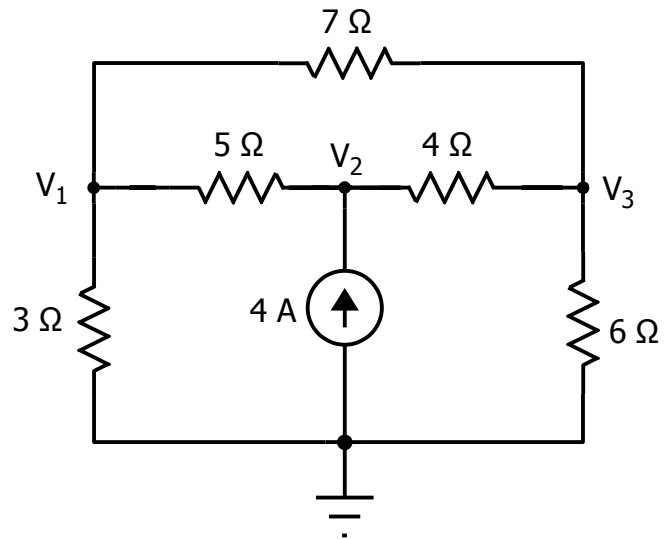8. This is almost the circuit that we studied in Problem 1. This time, we have replaced the battery with a current source. Find the three voltages. You may need to dig a little to work this problem.



$$\frac{V_1 - V_2}{5} + \frac{V_1}{3} + \frac{V_1 - V_3}{7} = 0$$

$$\frac{V_2 - V_1}{5} - 4 + \frac{V_2 - V_3}{4} = 0$$

$$\frac{V_3 - V_1}{7} + \frac{V_3 - V_2}{4} + \frac{V_3}{6} = 0$$

$$21V_1 - 21V_2 + 35V_1 + 15V_1 - 15V_3 = 0$$

$$4V_2 - 4V_1 - 80 + 5V_2 - 5V_3 = 0$$

$$24V_3 - 24V_1 + 42V_3 - 42V_2 + 28V_3 = 0$$

$$71V_1 - 21V_2 - 15V_3 = 0$$

$$-4V_1 + 9V_2 - 5V_3 = 80$$

$$-24V_1 - 42V_2 + 94V_3 = 0$$

$$V_1 = 7.2 \text{ V}$$

$$V_2 = 17.4 \text{ V}$$

$$V_3 = 9.6 \text{ V}$$