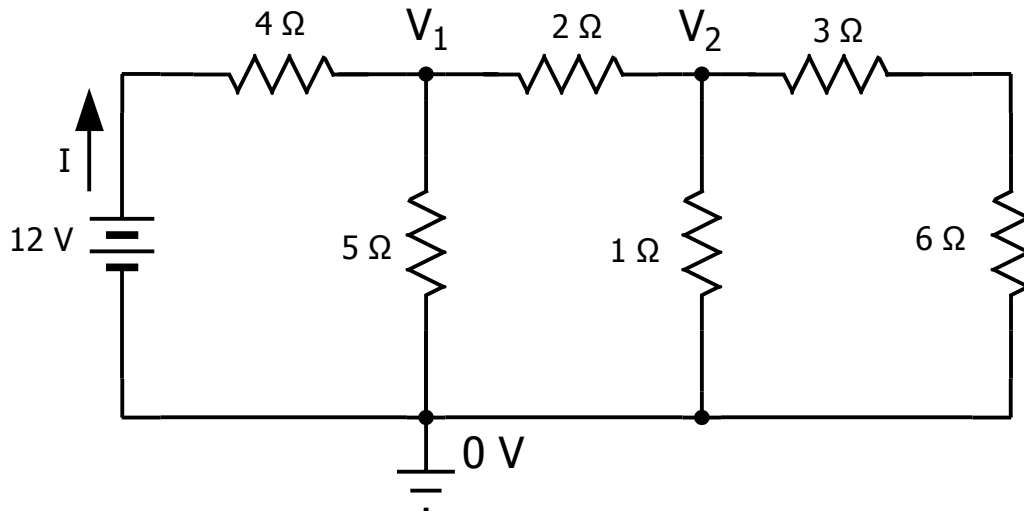


## EE3 Fall 2021

### Practice Problems 2




1. This is a similar circuit to that in Lecture1. Only the resistor values are different. It can be solved using series-parallel equivalents. But solve it using the NVA process below.
  - a. Assuming that all of the currents at Node 1 (where  $V_1$  is) are \*leaving\* the node, write an Ohm's Law expression for the current going through the  $4\ \Omega$  resistor.
  - b. Under the same assumption, write an Ohm's Law expression for the current through the  $5\ \Omega$  resistor.
  - c. Continuing, write an expression for the current through the  $2\ \Omega$  resistor.
  - d. Now, following the same procedure, write Ohm's Law expressions for the three currents leaving Node 2.
  - e. Now, combine the answers to 1a,b,c into a KCL equation.
  - f. Combine the three answers to 1d into a KCL equation.
2. You now have 2 equations in 2 unknowns. Solve them for  $V_1$  and  $V_2$ .
3. Now that you know  $V_1$ , you can compute  $I$ .

2.  $V_1 = 3.7744\text{ V}; V_2 = 1.1714\text{ V}$


3.  $I = 2.06\text{ A}$

## EE3 Fall 2021 Practice Problems 2

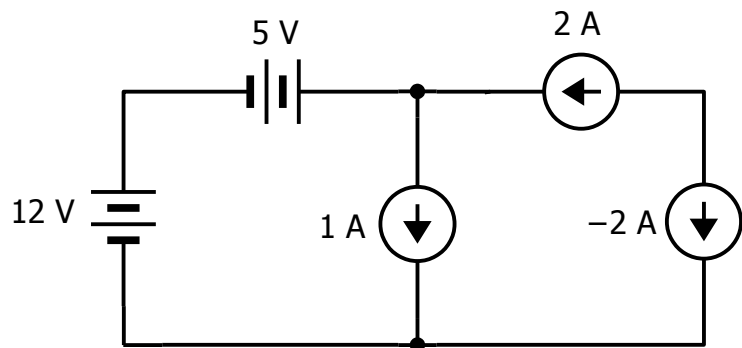4. Is this a "legal" circuit? If not, why not?



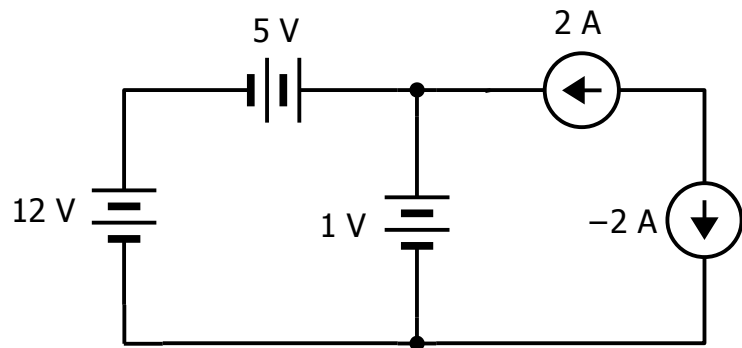
5. Is this a "legal" circuit? If not, why not?



## EE3 Fall 2021 Practice Problems 2


6. Using your knowledge of Node Voltage Analysis (NVA), find the current  $I$ .

$$I = 2.24 \text{ A}$$

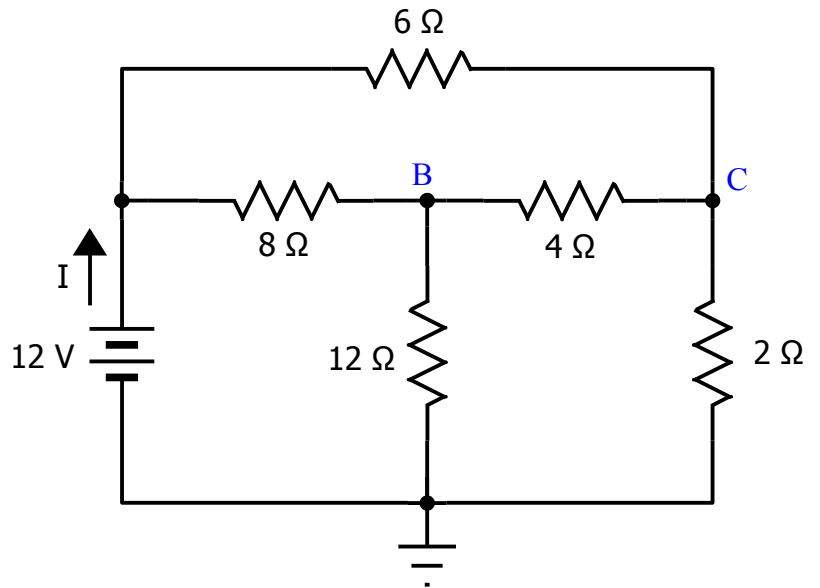

## EE3 Fall 2021 Practice Problems 2

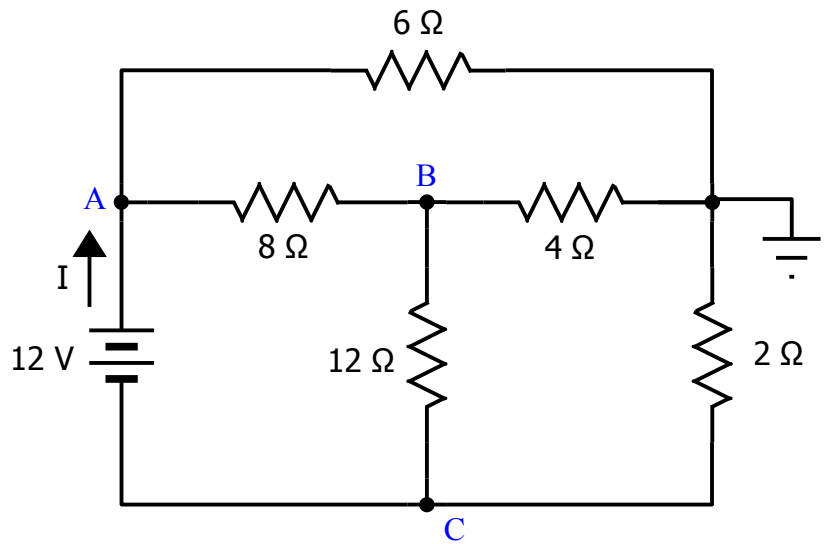7. This is the same circuit as Problem 6. Using your knowledge of Node Voltage Analysis (NVA), find the current  $I$ . HINT: Use  $I$  as an unknown fourth variable. (Note: with the reference node at a different location, you now have 3 unknown nodes. But you also know the voltage relationship between 2 of them.)




$$I = 2.24 \text{ A}$$

## EE3 Fall 2021

### Practice Problems 2

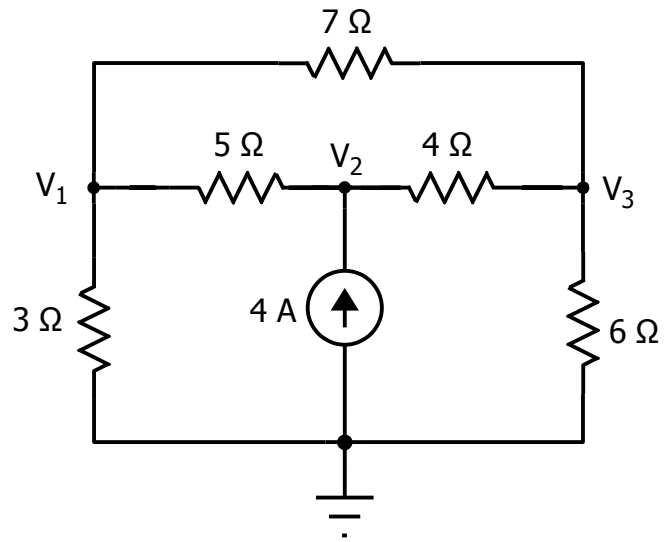8. This is almost the circuit that we studied in Problem 1. This time, we have replaced the battery with a current source. Find the three voltages. You may need to dig a little to work this problem.



$$\begin{aligned}V_1 &= 7.2 \text{ V} \\V_2 &= 17.4 \text{ V} \\V_3 &= 9.6 \text{ V}\end{aligned}$$