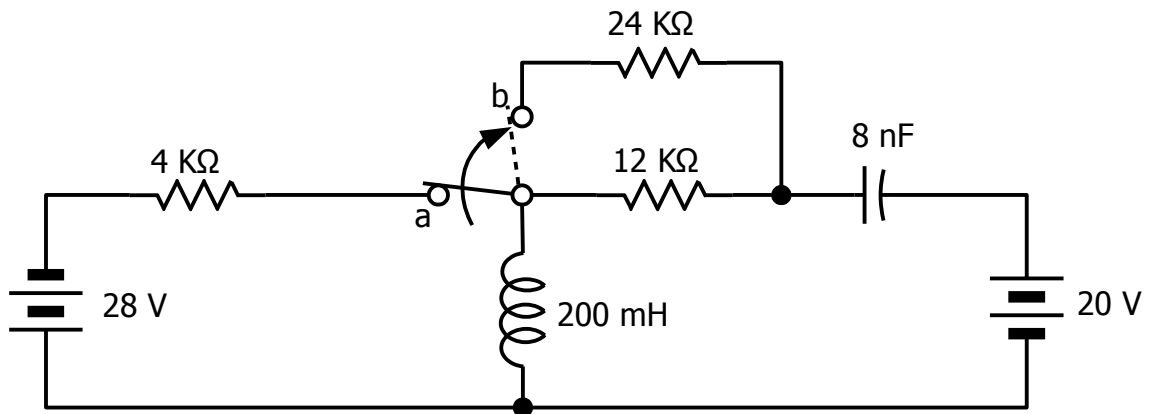



# EE3 Fall 2017

## Final Exam Practice Problems



1. The switch has been in position a for a long time. All transients have died out. At  $t = 0$ , the switch moves instantaneously to position b.
  - a. At  $t=0^-$  (the last instant that the switch is in position a), what is the current through the capacitor?  $0\text{ A}$
  - b. At  $t=0^-$  (the last instant that the switch is in position a), what is the voltage across the capacitor?  $-20 + v_C(0^-) + 0 + 0 = 0; v_C(0^-) = 20\text{ V, + at rt end}$
  - c. At  $t=0^+$  (the first instant that the switch is in position b), what is the current through the capacitor?  $I_C(0^+) = 28\text{ V} / 4\text{ K}\Omega = 7\text{ mA (L to R)}$
  - d. At  $t=0^+$  (the first instant that the switch is in position b), what is the voltage across the inductor?
  $\text{KVL CW: } v_C(0^+) + 20 - v_L(0^+) + (8\text{K})(7\text{mA}) = 0; v_L(0^+) = +56\text{ V; + at top}$
  - e. When the switch has been in position b for a long time, what is the voltage across the inductor?  $0\text{ V}$
  - g. When the switch has been in position b for a long time, what is the voltage across the capacitor?  $20\text{ V, + at right end}$
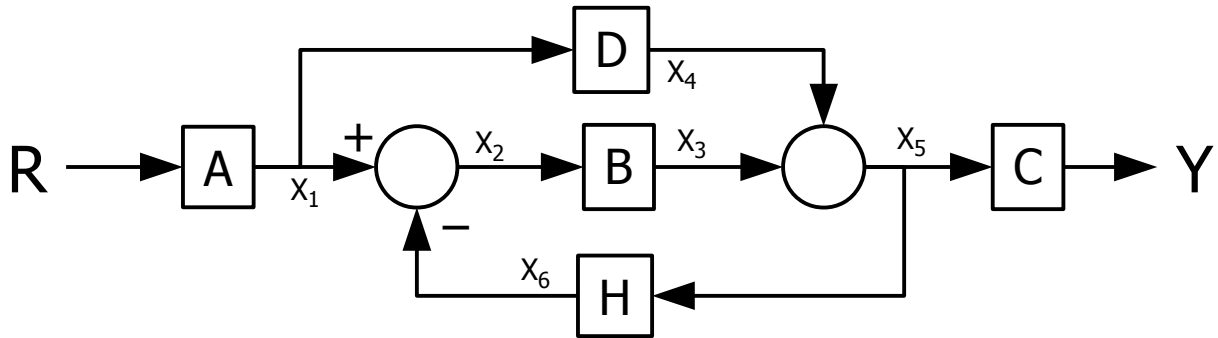
## EE3 Fall 2017 Final Exam Practice Problems



2. Find the transfer function  $Y/R$  (this will be a function of  $A$ ,  $B$ ,  $C$ ,  $D$ , and  $H$ ). Hint: assign a name, such as  $X_1$ , to the output of each block. Then find the expression for each block output. After that, it's algebra.

$$X_1 = AR$$

$$X_2 = X_1 - X_6$$

$$X_3 = BX_2 = BX_1 - BX_6 = ABR - BX_6$$

$$X_4 = DX_1 = ADR$$

$$X_5 = X_3 + X_4 = ABR - BX_6 + ADR$$

$$X_6 = HX_5 = H(ABR - BX_6 + ADR) = ABHR - BHX_6 + ADHR$$

$$X_6(1 + BH) = ABHR + ADHR$$

$$X_6 = \frac{ABHR + ADHR}{1 + BH} = \left( \frac{ABH + ADH}{1 + BH} \right) R$$


$$Y = CX_5 = C(ABR - BX_6 + ADR) = ABCR - BCX_6 + ACDR$$

$$Y = (ABC)R - \left[ BC \left( \frac{ABH + ADH}{1 + BH} \right) \right] R + (ACD)R$$

$$\frac{Y}{R} = ABC - \left( \frac{ABCH}{1 + BH} \right) (B + D) + ACD$$

## EE3 Fall 2017

### Final Exam Practice Problems

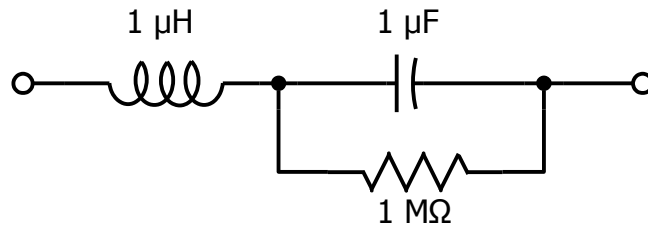


3. This is a more-realistic model of a  $1\ \mu\text{F}$  capacitor. The capacitor leads have inductance ( $1\ \mu\text{H}$ ), and the dielectric between the capacitor plates is less than perfect ( $1\ \text{M}\Omega$ ). Find the frequency where the capacitor stops being a capacitor and starts being an inductor (AKA the series resonant frequency).

At the resonant frequency  $\omega_0$ ,  $X_L = X_C$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1\text{e}6\ \text{rad/s}$$

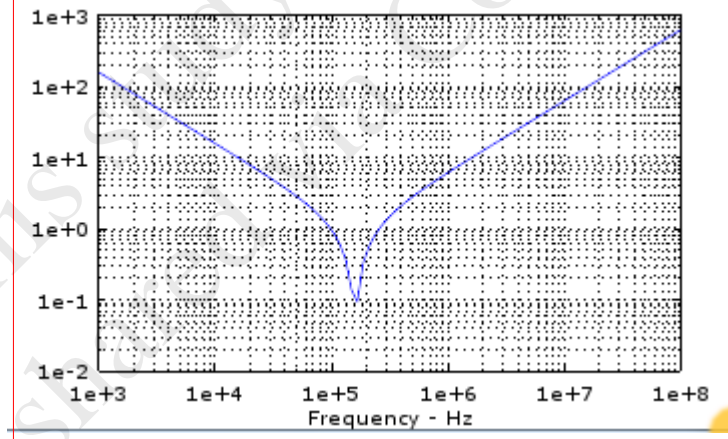
$$f_0 = \frac{\omega_0}{2\pi} = 159\ \text{KHz}$$



## EE3 Fall 2017

### Final Exam Practice Problems

4. This is a second-order circuit. There is an initial voltage on the capacitor (assuming clockwise current)  $v_C(0^-) = +12$  V, and an initial current in the inductor  $i_L(0^-) = 30$  mA clockwise. In order to solve the differential equation for  $i(t)$ , the initial voltages  $v_C(0^+)$  and  $v_R(0^+)$ , and  $di(t)/dt|_{t=0^+}$  must be found. Using what you know about inductors, capacitors, and KCL, find these values.

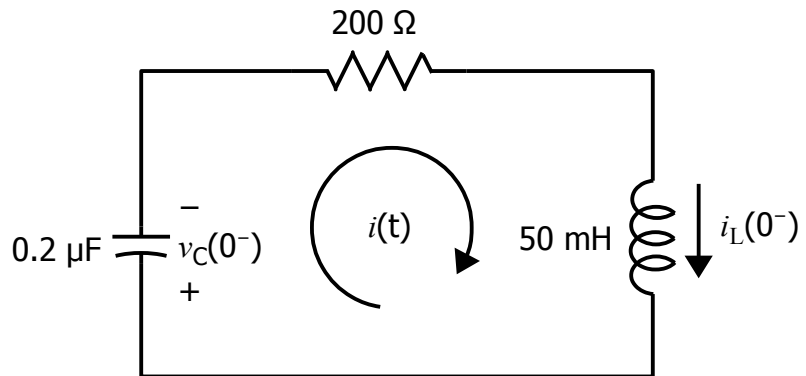


$$\begin{aligned}
 i(0^+) &= i_L(0^-) = 30 \text{ mA} \\
 v_C(0^+) &= v_C(0^-) = 12 \text{ V} \\
 v_R(0^+) &= i(0^+) R = 0.030 \cdot 200 = 6 \text{ V, + to left} \\
 \text{KVL@} t=0^+ &: +6 + 12 + v_L(0^+) = 0 \\
 v_L(0^+) &= -18 \text{ V} \\
 \text{Because } v_L(0^+) &= L \frac{di(t)}{dt} \Big|_{t=0^+} \\
 \frac{di(t)}{dt} \Big|_{t=0^+} &= \left( \frac{1}{0.05} \right) \cdot (-18) = -360 \text{ A/s}
 \end{aligned}$$

# EE3 Fall 2017

## Final Exam Practice Problems

5. Find the power dissipated by the  $5\ \Omega$  resistor.

9.47 W

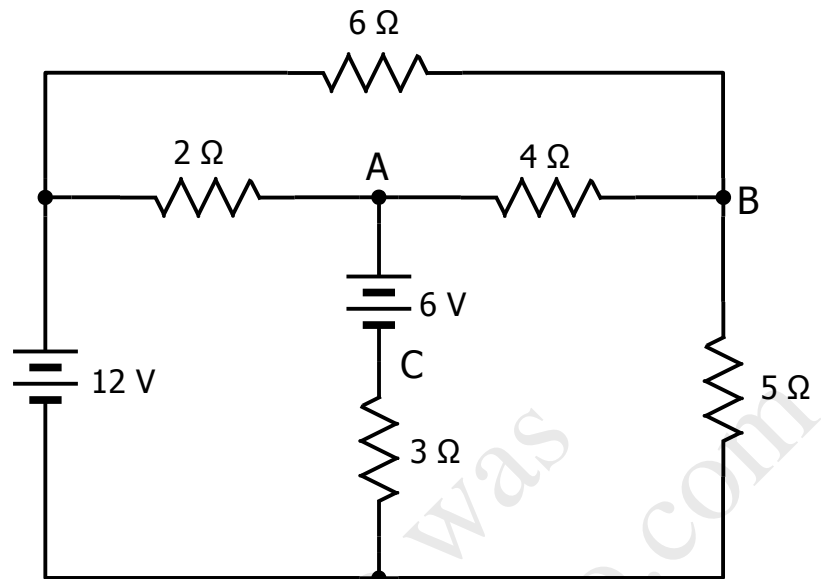

$$\frac{V_A - 12}{2} + \frac{V_C}{3} + \frac{V_A - V_B}{4} = 0$$

$$\frac{V_B - V_A}{4} + \frac{V_B}{5} + \frac{V_B - 12}{6} = 0$$

$$V_C = V_A - 6$$

$$0.75V_A - 0.25V_B + 0.333V_C = 6$$

$$-0.25V_A + 0.617V_B = 2$$

$$V_A - V_C = 6$$

$$V_A = 8.97\text{ V}$$

$$V_B = 6.88\text{ V}$$


$$V_C = 2.97\text{ V}$$

$$P_5 = \frac{(V_B)^2}{5} = \frac{6.88^2}{5} = 9.47\text{ W}$$

# EE3 Fall 2017

## Final Exam Practice Problems

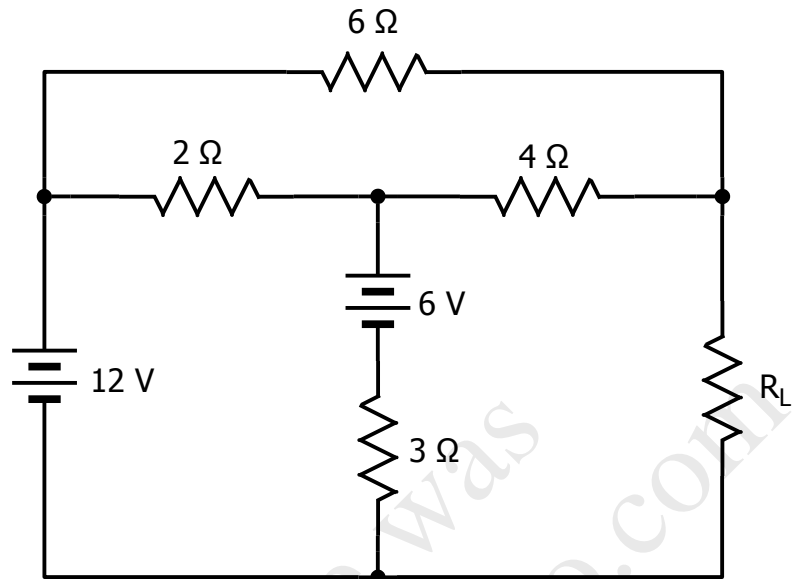6. Find the value of  $R_L$  for maximum power transfer to  $R_L$ .



Find the Thévenin Equivalent Resistance.

Open Circuit Voltage

$$V_1 = 12$$

$$\frac{V_2 - 12}{2} + \frac{V_2 - 6}{3} + \frac{V_2 - V_{OC}}{4} = 0$$

$$\frac{V_{OC} - V_2}{4} + \frac{V_{OC} - 12}{6} = 0$$

$$6V_2 - 72 + 4V_2 - 24 + 3V_2 - 3V_{OC} = 0$$

$$-3V_2 + 3V_{OC} + 2V_{OC} - 24 = 0$$

$$13V_2 - 3V_{OC} = 96$$

$$-3V_2 + 5V_{OC} = 24$$

$$V_2 = 9.8571 \text{ V}$$

$$V_{OC} = 10.7143 \text{ V}$$

Short Circuit Current

$$\frac{V_1 - 12}{2} + \frac{V_1 - 6}{3} + \frac{V_1}{4} = 0$$

$$V_1 = 7.3846 \text{ V}$$

$$I_4 = \frac{V_1}{4} = 1.8462 \text{ A}$$

$$I_6 = \frac{12}{6} = 2 \text{ A}$$

$$I_{SC} = I_4 + I_6 = 3.8462 \text{ A}$$

$$R_{\max\_pwr} = R_{th} = \frac{V_{OC}}{I_{SC}} = 2.79 \text{ } \Omega$$

2.79  $\Omega$