

# EE3 Fall 2021

## Homework Problem 3

Find the Thévenin Equivalent of this circuit.

