

ECE3 Fall 2021

Homework 4

Find the voltage v_2 .

HINT #1: study the Source Transformations section of Lecture 6. There is a way to make this problem much simpler.

HINT #2: all of the circuit calculations you learned for DC circuits also work for AC circuits. The only difference is that the numbers are complex instead of real.

