

The AD2's Impedance Analyzer has a source of error we do not account for here (one that is not present when using a DMM). What is this error and what information do we need to minimize it?

ANSWER HERE:

The resistance of the wires causes a slight error. We measured a  $2200\ \Omega$  resistor and in reality it was  $2306\ \Omega$ . There was an error of  $106\ \Omega$ . To minimize this error, we should choose a resistor with a lower tolerance level.

Note: For the remainder of this lab, disregard this error (i.e. treat the Impedance Analyzer's measurements as truth).

### Resistor Standard Values vs Tolerance

1. Pick 3 resistors with different color codes. If your resistors have 5 bands, consider only the first four bands. Measure their values with your AD2. Compare their stated values and tolerances (color code) with your measured analyzer results. (Do not exceed  $R_{ref}$  by a factor of 10)

<u>WORK SHEET HERE:</u>				
Resistor #	Marked	<u>MEASURED-MARKED</u> (100%)		
		AD2 Measured	% Deviation from Marked	Tolerance
R <sub>1</sub>	<u><math>100\ \Omega</math></u>	<u><math>95.1\ \Omega</math></u>	<u><math>-4.9\%</math></u>	<u><math>\pm 5\%</math></u>
R <sub>2</sub>	<u><math>3.3K\ \Omega</math></u>	<u><math>3.36K\ \Omega</math></u>	<u><math>1.8\%</math></u>	<u><math>\pm 5\%</math></u>
R <sub>3</sub>	<u><math>220\ \Omega</math></u>	<u><math>219.1\ \Omega</math></u>	<u><math>-0.41\%</math></u>	<u><math>\pm 5\%</math></u>

Is the % Deviation greater or less than the indicated tolerance?

ANSWER HERE:

They were all less than the indicated tolerance.



2. If you look at a standard list of 20% resistors available, you will see 1000 ohms and 1500 ohms but not 1200 ohms. Why? If you look at 5% resistors, would the results be different? Why? [An explanation of resistor values can be found at [this site](#). Be sure to watch the video. Also, [here](#).] Hint: Think about what tolerance means and how it differs from measurement error.

ANSWER HERE: With a  $\pm 20\%$  tolerance, a given resistor can cover a large range of values. For instance, the 1000 ohm resistor could read from 800 - 1200  $\Omega$  and the 1500  $\Omega$  resistor could read from 1200 - 1800  $\Omega$ . The overlap is redundant for 20% resistors. For 5%, the gap is less

3. Pick two resistors that are approximately two orders of magnitude different e.g. 22  $\Omega$  and 2,200 (See Figures 1-2, 1-3, and 1-4. Do not exceed  $R_{ref}$  by a factor of 10)
- a. Measure them carefully. Note their actual values rather than the color code indicated value.
- b. Measure them in series and parallel connections.

WORK SHEET HERE:

$R_1$  Measured Value: 21.7  $\Omega$

$R_2$  Measured Value: 2306  $\Omega$

$R_{Series}$  Value: 2327  $\Omega$

$R_{Parallel}$  Value: 21.3

- c. Compare  $R_{series}$  to the two individual resistors. Then compare  $R_{parallel}$  to the two individual resistors.
- d. In the series connection, which resistor dominates the resistance measurement and why? Try to explain without using the equation.
- e. In the parallel connection, which resistor dominates the resistance measurement and why? Try to explain without using the equation.

ANSWERS HERE:

- d) The resistor with the larger resistance dominates. Series is an addition, so it makes sense the larger addend (resistor) dominates.
- e) The resistor with the lesser resistance dominates. The voltage will follow the path of least resistance.



WORK SHEET HERE:

Record your measurement  $v_{R1}$  at Channel 1: -3.495V

Solve for the current  $i$  (use labeled resistances): 0.0156A

Calculate  $R1$ 's power as:  $v_{R1} * i =$  -0.055


$$V = iR$$

3. Passive Sign Convention is a standard rule in circuit theory that denotes what the sign of a component's power is when it either absorbs or generates energy. Under this convention, a positive sign for power means a component is absorbing energy while a negative sign for power means a component is generating energy.

If the previous steps were followed correctly, you will find that the calculated power for  $R1$  does not make sense using Passive Sign Convention. Why does it not make sense (hint: notice how  $R1$  is warm) and how can you correct this calculation?

ANSWER HERE:

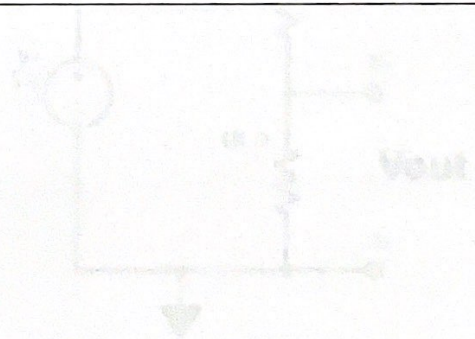The  $1^+$  and  $1^-$  in the circuit diagram are swapped. This caused the voltage to be negative. This made the power be negative when it should be positive. To fix this, swap the  $1^+$  and  $1^-$ .





## Unloaded and Loaded Voltage Dividers

We will investigate the effect that loading has on a voltage divider circuit. Loading, as you recall from lecture, is the demand for current from a voltage source. That demanded current has an effect on the performance of the circuit. We will be measuring the amount of that performance change.

You will need the following components:


1 K $\Omega$  resistors (2)

3.3 K $\Omega$  resistor

Breadboard

AD2

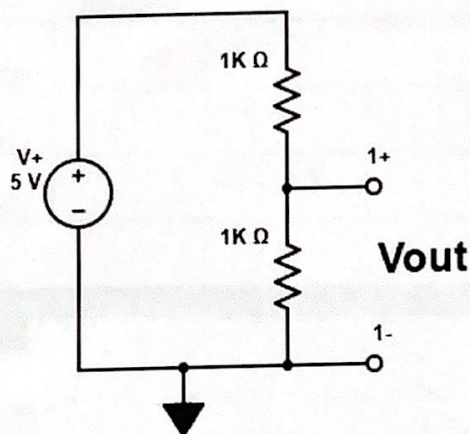
1. Construct the voltage divider circuit as shown below. This is an unloaded voltage divider.



2. Measure  $V_{out}$  at Channel 1 as shown. Record the value here 2.51 V.



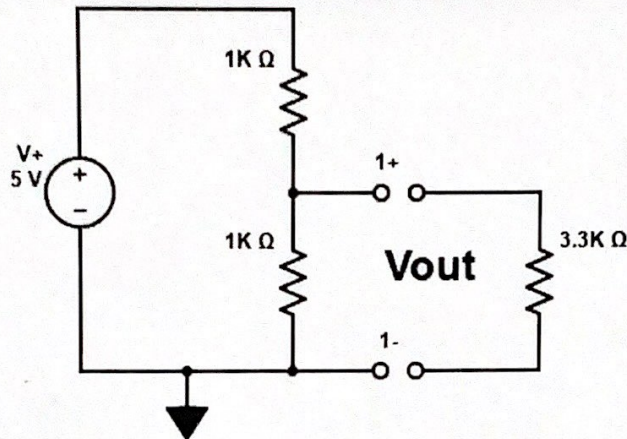3. Now load the circuit by attaching the  $3.3\text{ K}\Omega$  load resistor across the lower  $1\text{ K}\Omega$  resistor, as shown below. The  $3.3\text{ K}\Omega$  resistor is now demanding current from the voltage divider.



4. Measure the new  $V_{out}$  as in Step 2. Record the value here: 2.182 V  
 5. Fill out the following table:

	UNLOADED VOLTAGE DIVIDER	LOADED VOLTAGE DIVIDER
$V_{out}$ (measurement)	2.51 V	2.182 V
$V_{upper 1K}$ (calculation)	2.49 V	2.818 V
$I_{total}$ (calculation)	0.0025 A	0.0028 A

$$V_x = V_o \frac{R_1}{R_1 + R_2}$$

$$V = IR$$

$$5 = I(1767)$$

Why does an increase in total current result in lower output voltage of the loaded voltage divider circuit?

$$V = IR$$

The lower resistance from the parallel resistors outweighs the significance of the increase in current. This causes voltage to actually decrease. With a greater amount of current, the first resistor consumes more voltage. This causes the voltage for the second resistor to decrease.