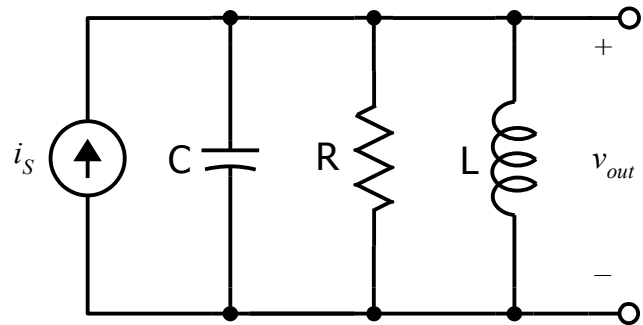


# EE3 Fall 2021

## Practice Problems 6

1. Find the impedance  $Z_{tot}$  presented by the RLC network to the current source. This is a symbolic exercise (no numbers).



a. What is  $Z_{tot}$  when  $\omega=0$ ?

b. What is  $Z_{tot}$  when  $\omega \rightarrow \infty$ ?

c. What is  $Z_{tot}$  when  $\omega = \frac{1}{\sqrt{LC}}$ ?

d. What does the answer to (c.) tell you about the parallel combination of L&C when  $\omega = \frac{1}{\sqrt{LC}}$ ?

$$\begin{aligned}
 Z_{tot} &= \frac{1}{j\omega C + \frac{1}{R} + \frac{1}{j\omega L}} \\
 &= \frac{1}{j\omega C + \frac{R + j\omega L}{j\omega RL}} \\
 &= \frac{j\omega RL}{(R - \omega^2 RLC) + j\omega L} \\
 &= \frac{j\omega RL}{R(1 - \omega^2 LC) + j\omega L}
 \end{aligned}$$

$$a. Z_{tot}|_{\omega=0} = \frac{0}{R} = 0$$

$$b. Z_{tot}|_{\omega \rightarrow \infty} = \frac{jRL}{-2\omega LC + \omega L}|_{\omega \rightarrow \infty} = 0$$


$$c. Z_{tot}|_{\omega = \frac{1}{\sqrt{LC}}} = \frac{j\omega RL}{R(0) + j\omega L} = R$$

d.  $L||C$  at resonance has infinite impedance.  
 $L||C$  at resonance is called a *tank circuit*.

## EE3 Fall 2021

### Practice Problems 6

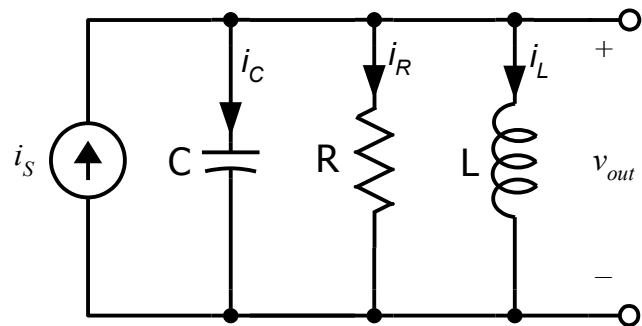2. Consider this circuit to be a filter, with an input and an output. To answer the following questions use the two-question intuitive approach described in lecture.




- If the input is  $i_s$  and the output is  $i_C$ , what kind of filter is this?
- If the input is  $i_s$  and the output is  $i_R$ , what kind of filter is this?
- If the input is  $i_s$  and the output is  $i_L$ , what kind of filter is this?
- If the input is  $i_s$  and the output is  $v_{out}$ , what kind of filter is this?

## EE3 Fall 2021

### Practice Problems 6

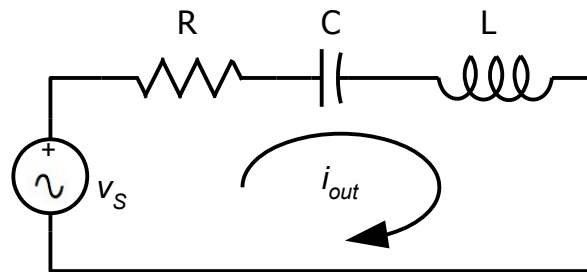3. Consider this circuit to be a filter, with an input and an output. To answer the following questions use the two-question intuitive approach described in lecture.




- If the input is  $v_s$ , and the output is  $v_C$ , what kind of filter is this?
- If the input is  $v_s$ , and the output is  $v_R$ , what kind of filter is this?
- If the input is  $v_s$ , and the output is  $v_L$ , what kind of filter is this?
- If the input is  $v_s$ , and the output is  $i_{out}$ , what kind of filter is this?

# EE3 Fall 2021

## Practice Problems 6

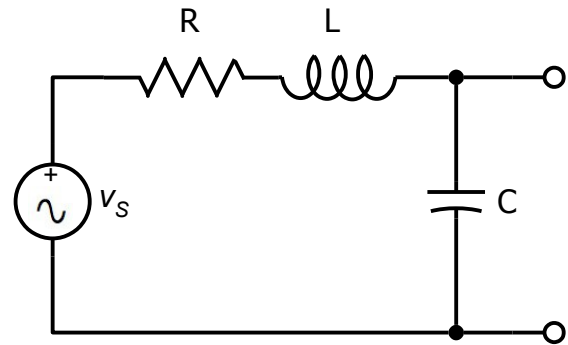4. Find the impedance  $Z_{tot}$  presented by the RLC network to the current source. This is a symbolic exercise (no numbers).



a. What is  $Z_{tot}$  when  $\omega=0$ ?

b. What is  $Z_{tot}$  when  $\omega \rightarrow \infty$ ?

c. What is  $Z_{tot}$  when  $\omega = \frac{1}{\sqrt{LC}}$ ?

d. What does the answer to (c.) tell you about the series combination of L&C when  $\omega = \frac{1}{\sqrt{LC}}$ ?

$$Z_{tot} = R + Z_L + Z_C = R + j\omega L - j\left(\frac{1}{\omega C}\right) = R + j\left(\omega L - \frac{1}{j\omega C}\right)$$

a.  $Z_{tot}|_{\omega=0} = R + j\{\rightarrow \infty\} \rightarrow \infty$

b.  $Z_{tot}|_{\omega \rightarrow \infty} = R + j\{\rightarrow \infty\} \rightarrow \infty$

c.  $Z_{tot}|_{\omega = \frac{1}{\sqrt{LC}}} = R + j0 = R$

d.  $L$  in series with  $C$  at resonance has zero impedance.  
Do you see the logical dual?