

Week 3: Transducers


It is **HIGHLY RECOMMENDED** that you read through this week's lab and familiarize yourself with all the material before attending the lab session—there is a lot of content in this week's lab and understanding the material is critical for success!

Week 3 Prelab

Briefly answer the following questions.

Name: Preetika UID: 204912895
Kirovedula

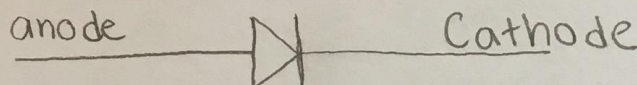1. Draw the circuit schematic symbol of a diode and label the anode and cathode.



2. When a diode is forward biased, the anode is at a (circle one) higher // lower voltage than the cathode.
3. When looking at the diode itself, what are the two methods for telling which side of an LED is the anode and which side is the cathode?
 1. The longer end is the anode and the shorter end is the cathode
 2. The rounded side is the anode and the flat side is the cathode
4. Fill in the blank: When a high voltage relative to the emitter is applied to the base of an NPN transistor, current is allowed to flow from the collector to the emitter.

Week 3 Prelab End