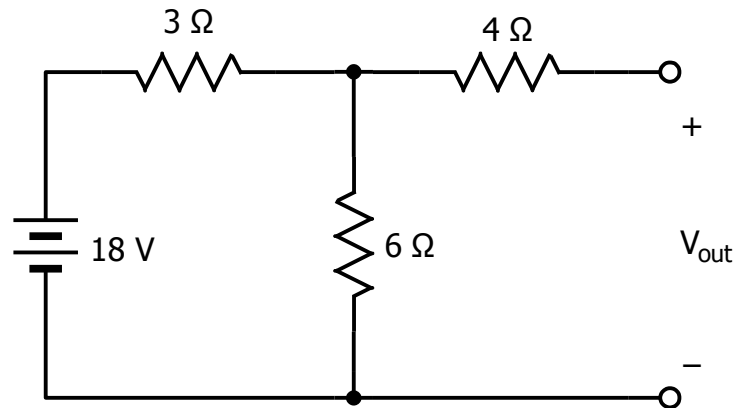


# EE3 Fall 2021

## Practice Problems 4

1. Find the Thévenin equivalent circuit for the given circuit, using all three methods discussed in lecture.



$$R_{th} = 6 \, \Omega$$


## EE3 Fall 2021

### Practice Problems 4

2a. Use Node Voltage Analysis to find  $V_{OC}$ .

Hint: find an expression for  $I_2$ .

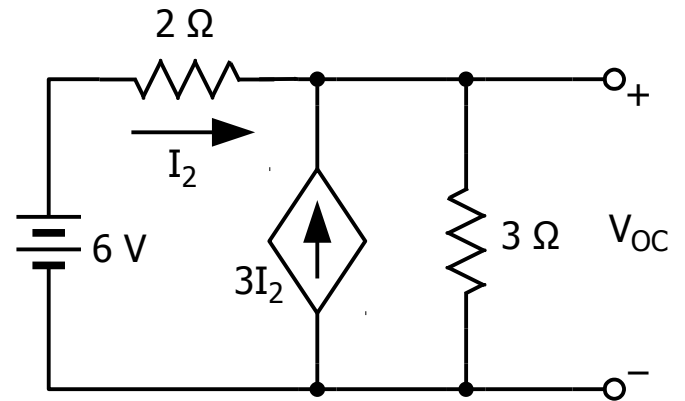2b. Use both allowable methods to find  $R_{th}$ .




$$R_{th} = 0.43 \, \Omega$$

# EE3 Fall 2021

## Practice Problems 4

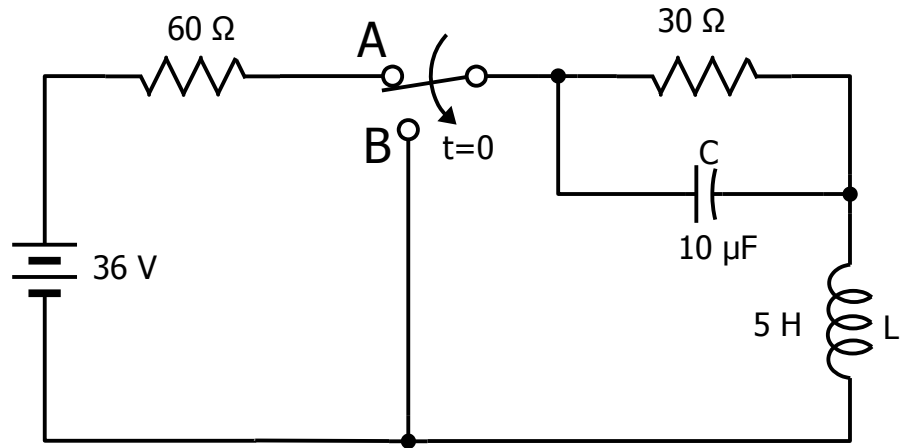3. The switch has been in position A for a LONG TIME before switching to position B at  $t = 0$ .

- Find magnitude & direction of  $i_L(0^-)$
- Find magnitude and polarity of  $v_C(0^-)$
- Find magnitude and polarity of  $v_L(0^+)$
- Find magnitude and direction of  $i_R(0^+)$
- Find magnitude and direction of  $i_C(0^+)$




$$i_C(0^+) = 0$$

# EE3 Fall 2021

## Practice Problems 4

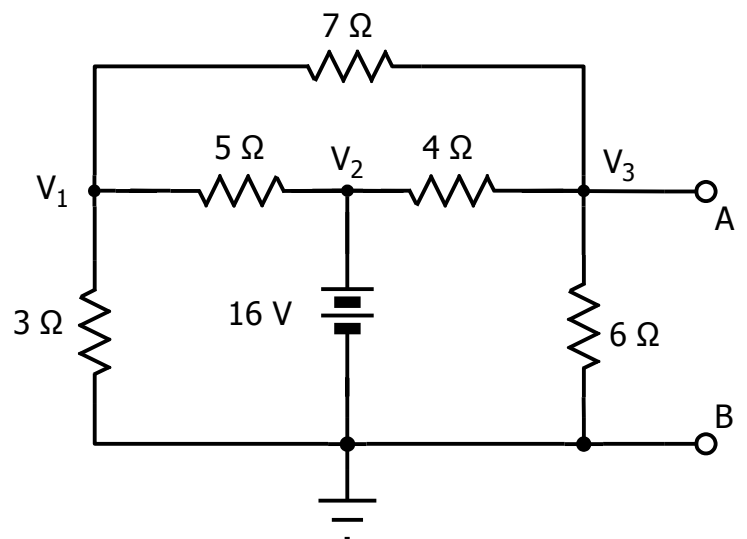- 4.
- Given the  $V_3 = 8.8 \text{ V}$ , use the  $V_{OC}$ - $I_{SC}$  method to find the Thévenin Equivalent circuit, looking in through Port A-B.
  - Compare your  $R_{th}$  to the answer in Problem 5.




$$R_{th} = 1.89 \Omega$$

# EE3 Fall 2021

## Practice Problems 4

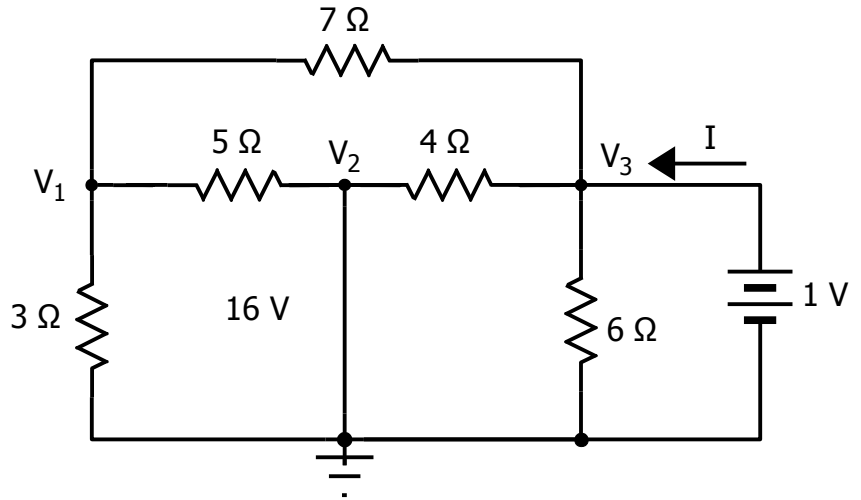5. This is the circuit that we studied in Problem 4. This time, you will find the Thévenin Equivalent circuit by using Method (b.).  $V_{oc}$  does not change. For  $R_{th}$ , we replaced the 16 V battery with a short and attached a 1 V battery to the circuit as shown.
- Find the current  $I$ .
  - Compute  $1\text{ V} / I$ . Units are ohms.
  - Compare your answer to Problem 4.




$$R_{th} = 1.89\ \Omega$$

## EE3 Fall 2021

### Practice Problems 4

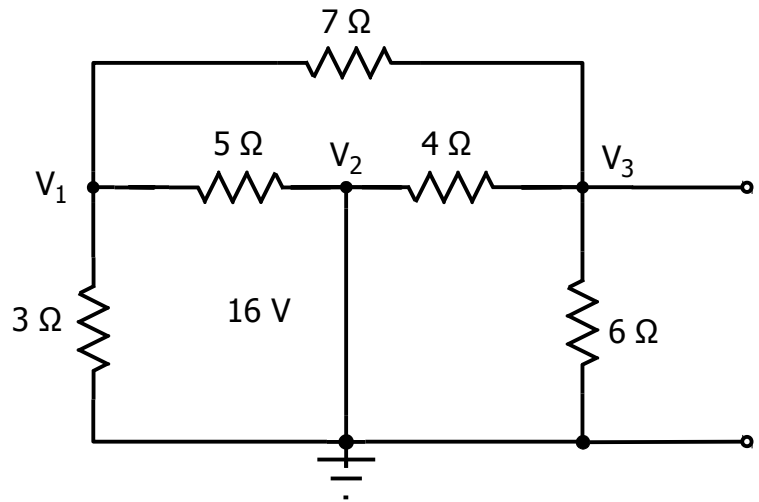6. This is the circuit that we studied in Problem 1. This time, you will find the Thévenin Equivalent circuit by using Method (c.). We replaced the 16 V battery with a short.
- Using your knowledge of series and parallel circuits, find the resistance of the circuit when looking in through the port.
  - Compare your answer to Problem 4.




$$R_{th} = 1.89 \, \Omega$$

# EE3 Fall 2021

## Practice Problems 4

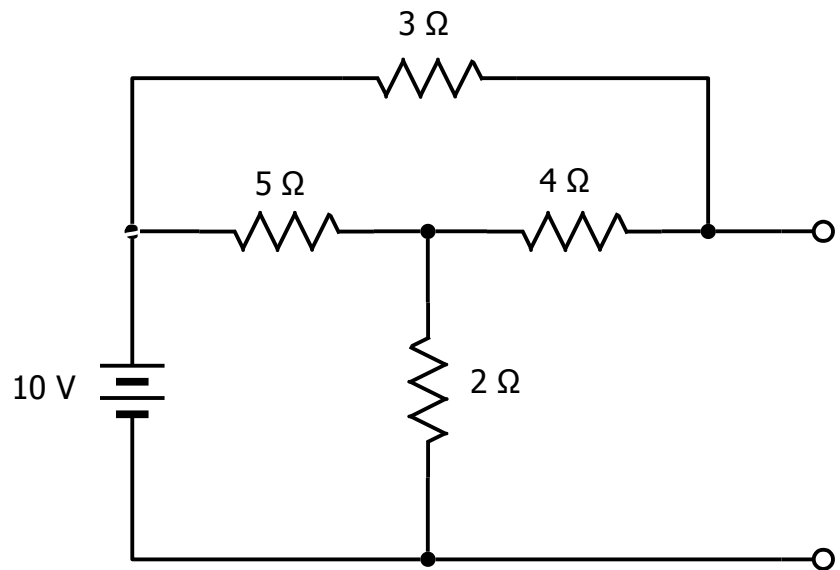7. Find the Thévenin Equivalent circuit, using Method a.




1.93Ω

# EE3 Fall 2021

## Practice Problems 4

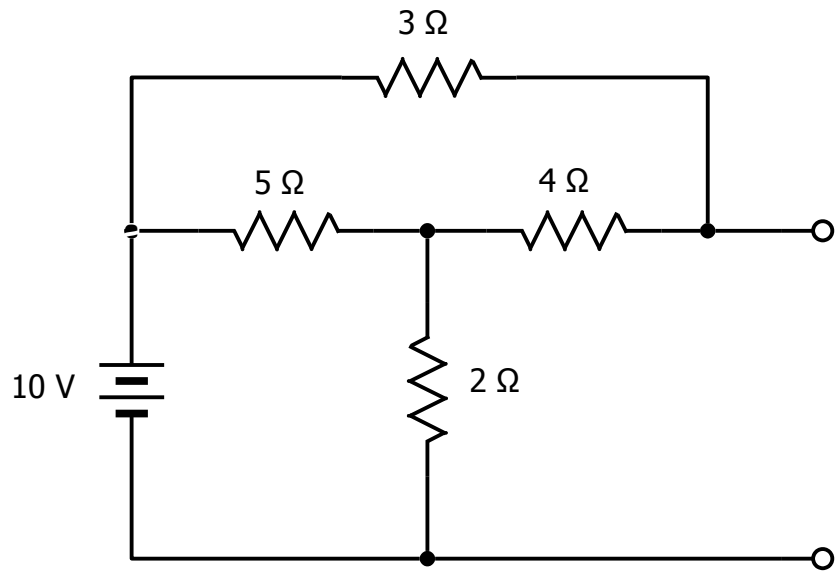8. Find the Thévenin  
Equivalent circuit, using  
Method c.



1.93 Ω