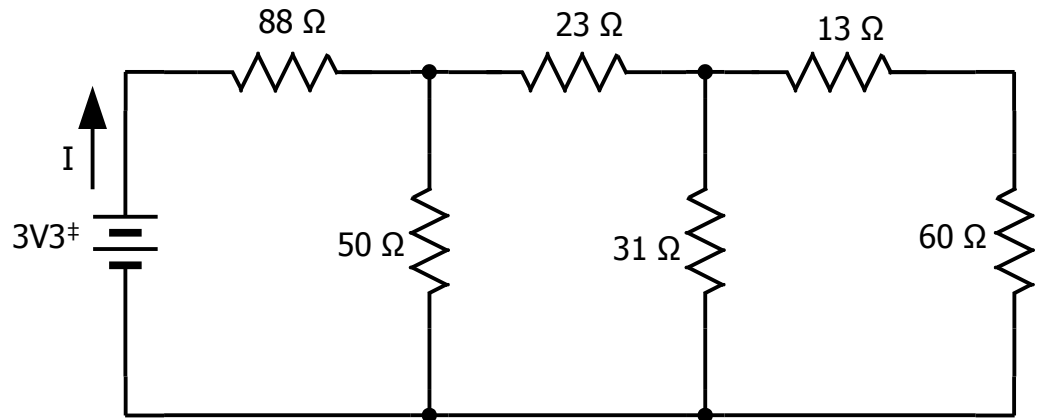


# ECE3 Summer 2021

## Practice Problems 1

1. Using your knowledge of series and parallel equivalents that you learned on p. 23 of the Week 1 lab, determine the current  $I$ .



60 Ω and 13 Ω are in series.

$$R_{eq1} = 60 + 13 = 73 \Omega$$

$R_{eq1}$  and 31 Ω are in parallel.

$$R_{eq2} = \frac{73 \cdot 31}{73 + 31} = 21.8 \Omega$$

$R_{eq2}$  and 23 Ω are in series.

$$R_{eq3} = 23 + 21.8 = 44.8 \Omega$$

$R_{eq3}$  and 50 Ω are in parallel.

$$R_{eq4} = \frac{44.8 \cdot 50}{44.8 + 50} = 23.6 \Omega$$

$R_{eq4}$  and 88 Ω are in series

$$R_{tot} = R_{eq4} + 88 = 111.6 \Omega$$


$$I = \frac{3.3 \text{ V}}{111.6 \Omega} = 0.0296 \text{ A}$$

‡ 3V3 is shorthand for 3.3 V. You will see this often on schematics.

# ECE3 Summer 2021

## Practice Problems 1

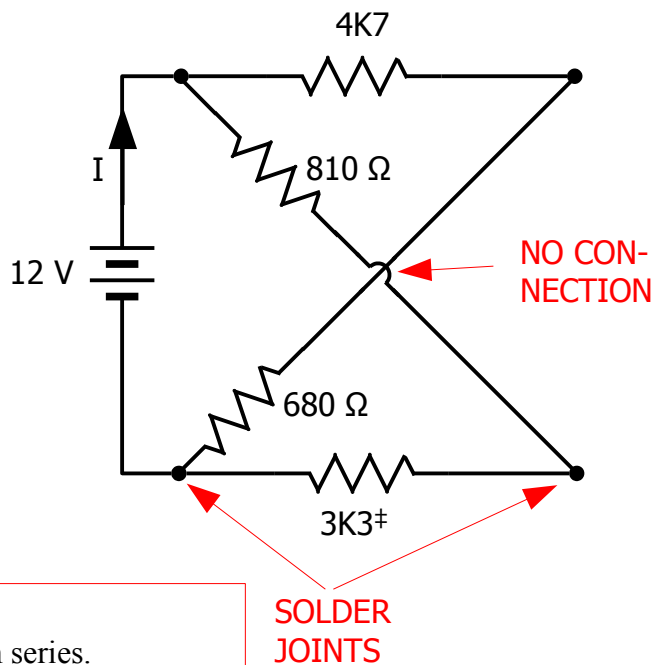2. Using your knowledge of series and parallel equivalents, determine the value of  $I$ .



4K7 and 680 Ω are in series. 3K3 and 810 Ω are in series.


$$4.7\text{e}3 + 0.68\text{e}3 = 5.38\text{e}3 \Omega$$

$$3.3\text{e}3 + 0.81\text{e}3 = 4.11\text{e}3 \Omega$$

$$5.38\text{e}3 \text{ and } 4.11\text{e}3 \text{ are in parallel. } R_p = \frac{5.38\text{e}3 \cdot 4.11\text{e}3}{9.49\text{e}3} = 2.33\text{e}3 \Omega$$

$$I = \frac{12}{2.33\text{e}3} = 0.00515 \text{ A} = 5.15 \text{ mA}$$

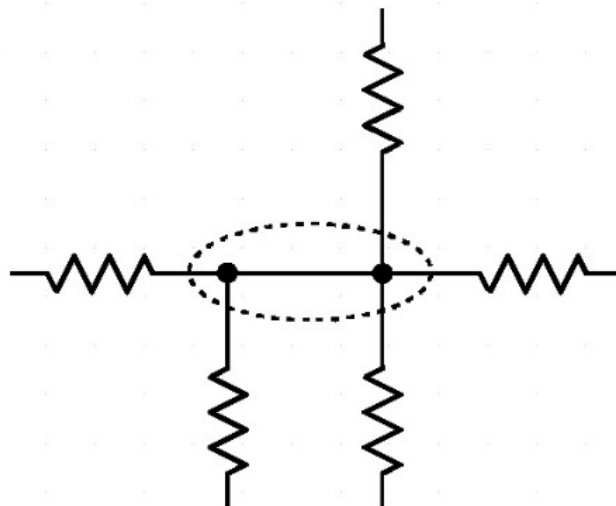3. This question may require a little digging on your part.



The circuit fragment inside the dotted ellipse is:


- Choose one answer.
- ☐ a. not a node
  - ☒ b. 1 node
  - ☐ c. 2 nodes

‡ 3K3 is shorthand for 3.3KΩ. You will see this often on schematics.

# ECE3 Summer 2021

## Practice Problems 1

4.

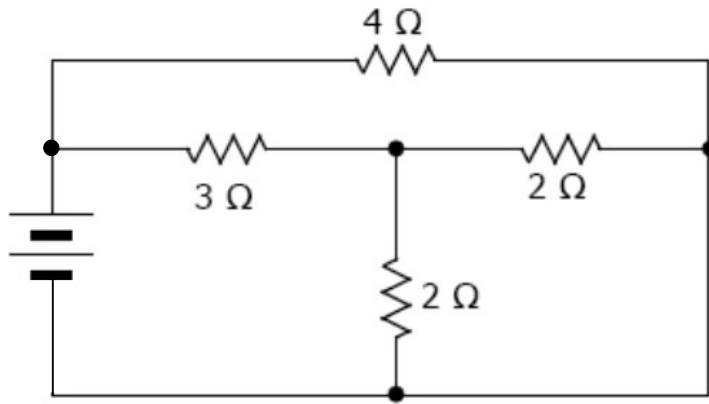

This circuit can be reduced to a voltage source and one resistor. What is the value of that one final resistor?

Challenge: try to do this one in your head: no paper/pencil, no calculator/computer. If you understand series and parallel, you can do it.

The two  $2\ \Omega$  resistors are in parallel. Therefore:

$$R_{22} = 1\ \Omega$$

$R_{22}$  and  $3\ \Omega$  resistor are in series.

$$R_{223} = 4\ \Omega$$

$R_{223}$  and  $4\ \Omega$  resistor are in parallel.

$$\text{So } R_{tot} = 4 \parallel 4 = 2\ \Omega$$




# ECE3 Summer 2021

## Practice Problems 1

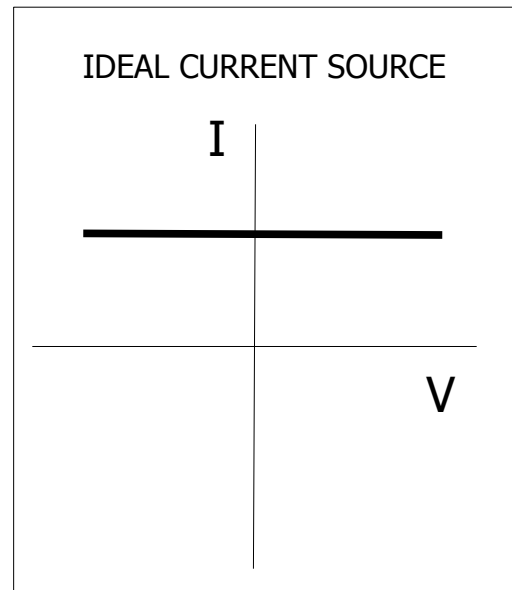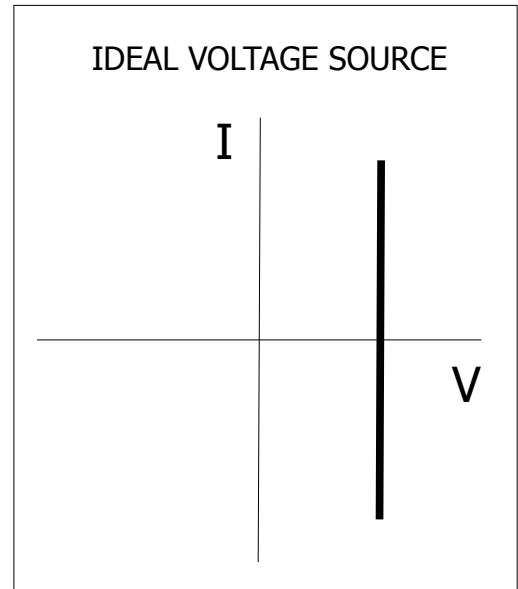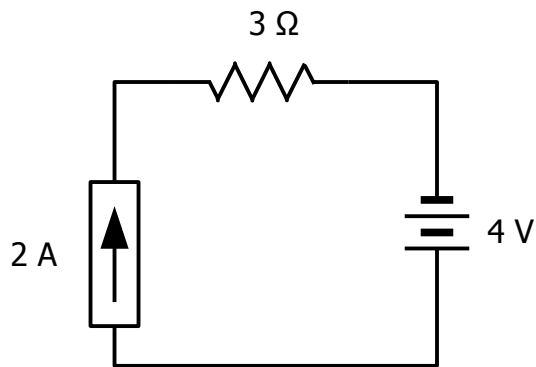5. Study the

[Khan Academy post on Passive Sign Convention.](#)

Then, using your knowledge of the I-V curves for voltage and current sources as explained in the YouTube videos, plus your knowledge of the Passive Sign Convention, determine if the 4 V battery is providing or absorbing power.




Providing; current is leaving the + end of the battery.

# ECE3 Summer 2021

## Practice Problems 1

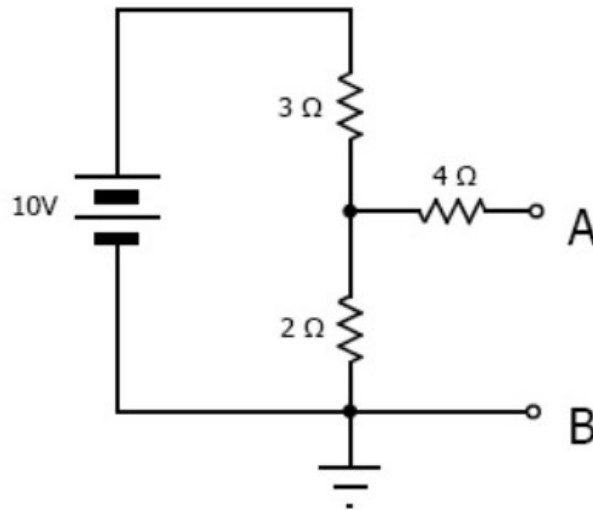6. What is the voltage across the  $4\ \Omega$  resistor? NOTE: you may consider this to be a trick question, but it has real meaning.


There can be no current through  $4\ \Omega$ .  
So there can be no voltage across  $4\ \Omega$ .



Choose  
one  
answer.

- ☐ a. 2.67 V
- ☒ b. 0.00 V
- ☐ c. 5.71 V
- ☐ d. 10.00 V
- ☐ e. 4.00 V

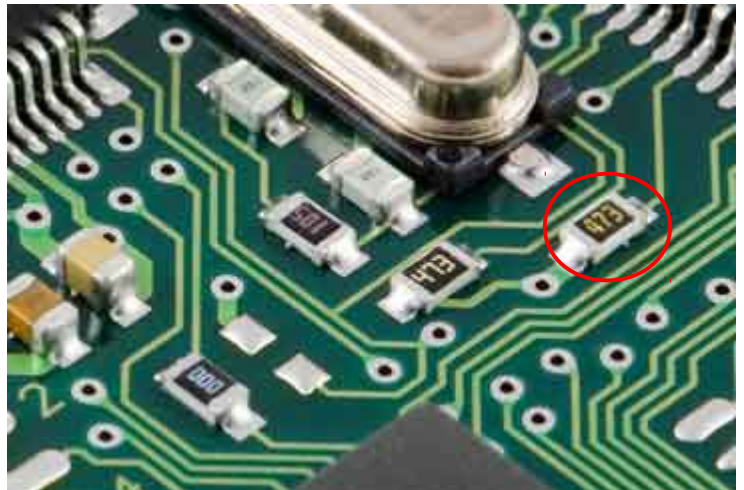7. This is the picture of a surface mount resistor (labeled 473) on a PC board. Assuming that the three numbers correspond to the first three colors of a regular resistor, what is the resistance of this surface mount resistor?




$47 \times 10^3$ , or 47 K $\Omega$

# ECE3 Summer 2021

## Practice Problems 1

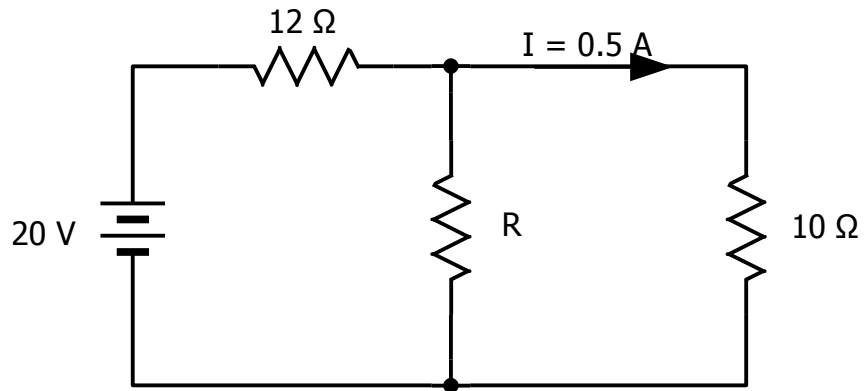8. Using your knowledge of series and parallel equivalents plus the Voltage Divider equation, determine the value of R.



$R$  and  $10\ \Omega$  are in parallel. Therefore.

$$R_p = \frac{10R}{10+R}$$

$R_p$  and  $12\ \Omega$  are in series

$$R_{tot} = 12 + R_p$$

By Voltage Divider Equation,

$$V_R = 20 \left( \frac{R_p}{12 + R_p} \right)$$

$$\text{But } V_R = I(10) = 5\ \text{V}$$

$$\text{So } \frac{R_p}{12 + R_p} = \frac{5}{20} = \frac{1}{4}$$

$$R_p = 4 = \frac{10R}{10+R}$$

$$R = 6.67\ \Omega$$