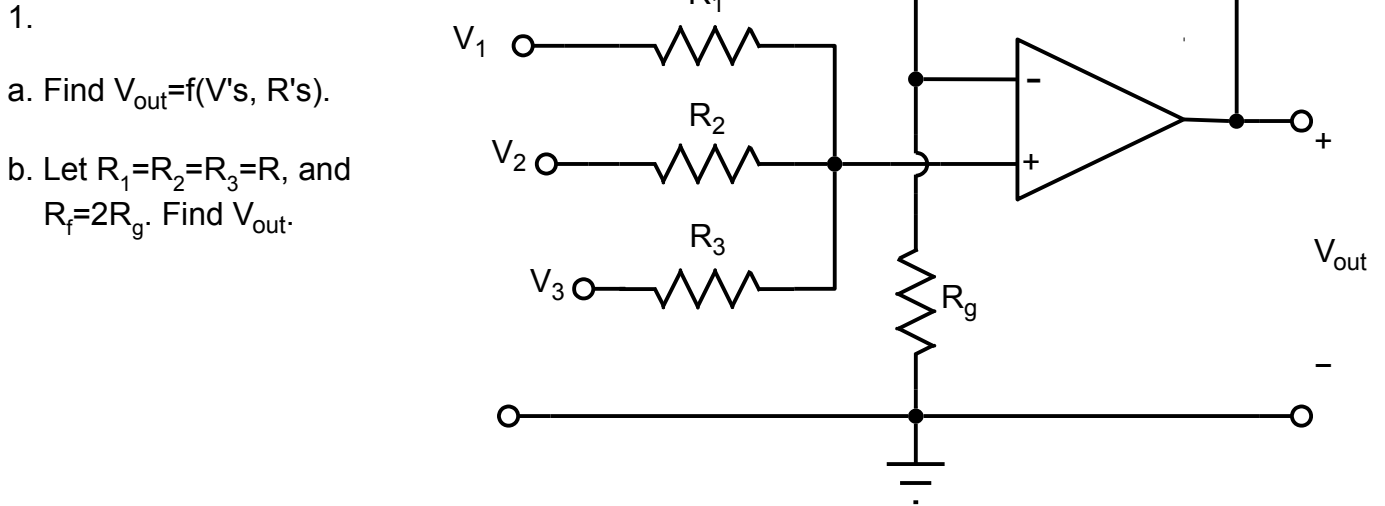


# ECE3 Fall 2021

## Practice Problems 7



$$\textcircled{1} \quad \frac{v_p - V_1}{R_1} + \frac{v_p - V_2}{R_2} + \frac{v_p - V_3}{R_3} + i_p = 0$$

$$\textcircled{2} \quad \frac{v_p - V_{out}}{R_f} + \frac{v_p}{R_g} = 0$$

$$\textcircled{1} \quad v_p \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\textcircled{2} \quad v_p \left( \frac{1}{R_f} + \frac{1}{R_g} \right) = \frac{V_{out}}{R_g}$$

$$\textcircled{2} \quad v_p = V_{out} \left( \frac{R_g}{R_f + R_g} \right)$$

$$\textcircled{1} \quad V_{out} \left( \frac{R_g}{R_f + R_g} \right) = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right)$$

$$V_{out} = \left( \frac{R_f + R_g}{R_g} \right) \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \left( \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)$$

If  $R_1 = R_2 = R_3 = R_i$  and  $R_f = 2R_g$ ,


$$V_{out} = (1+2) \left( \frac{V_1 + V_2 + V_3}{R_i} \right) \left( \frac{R_i^3}{3 R_i^2} \right)$$

$$V_{out} = V_1 + V_2 + V_3$$

## ECE3 Fall 2021 Practice Problems 7

2. Let  $R_4 = R_2$ , and  $R_3 = R_1$ . Find  $V_o = f(V_s, R's)$ . HINT: write 2 KCL equations at the input.

$$V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

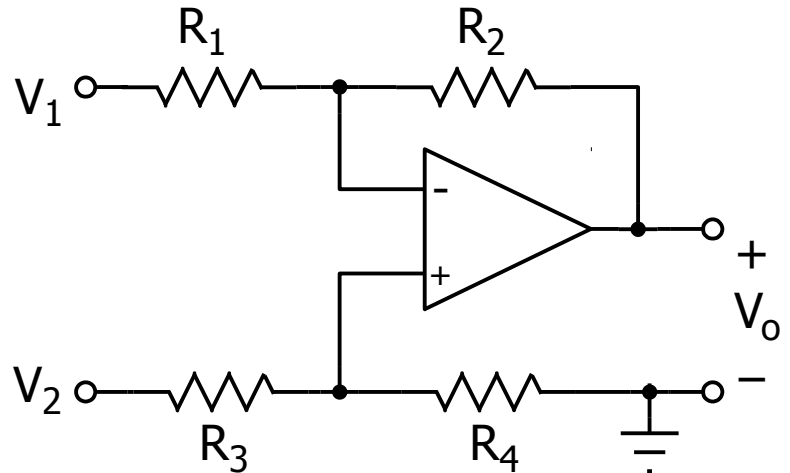

Write 2 KCL equations:

$$\frac{v_n - V_1}{R_1} + \frac{v_n - V_o}{R_2} = 0$$

$$\frac{v_p - V_2}{R_3} + \frac{v_p}{R_4} = 0$$

But  $R_3 = R_1$  and  $R_4 = R_2$ , so

$$\frac{v_n - V_1}{R_1} + \frac{v_n - V_o}{R_2} = 0$$

$$\frac{v_p - V_2}{R_1} + \frac{v_p}{R_2} = 0$$

$v_n$ ,  $v_p$ , and  $V_o$  are unknown, so we need a third equation.

$$v_p = v_n = v$$

$$\frac{v - V_1}{R_1} + \frac{v - V_o}{R_2} = 0 = \frac{v - V_2}{R_1} + \frac{v}{R_2}$$


$$\frac{-V_1}{R_1} - \frac{V_o}{R_2} = -\frac{V_2}{R_2}$$

$$V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

## ECE3 Fall 2021 Practice Problems 7

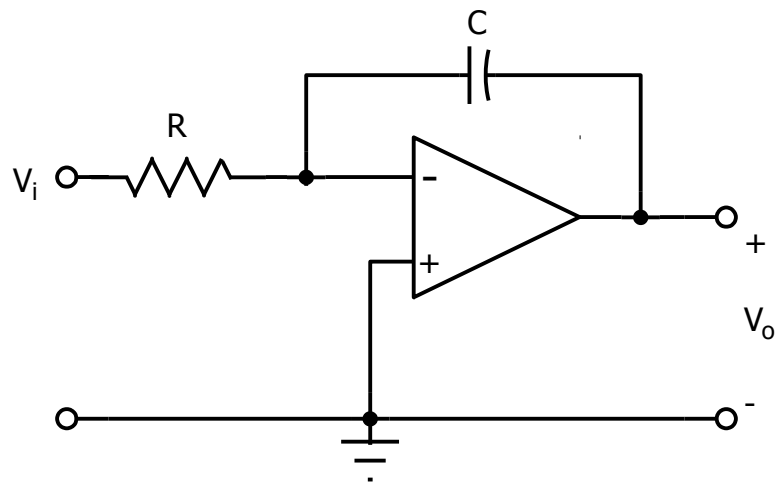3. This is something else that op amps do well. Find  $V_o$  as a function of  $V_i$ ,  $C$ , and  $R$ .


HINT: write a KCL equation at the inverting input.



$$\begin{aligned}\frac{0 - V_i}{R} + C \frac{d(0 - V_o)}{dt} &= 0 \\ \frac{dV_o}{dt} &= -\left(\frac{1}{RC}\right)V_i \\ V_o &= -\left(\frac{1}{RC}\right)\int V_i dt\end{aligned}$$

# ECE3 Fall 2021 Practice Problems 7

4

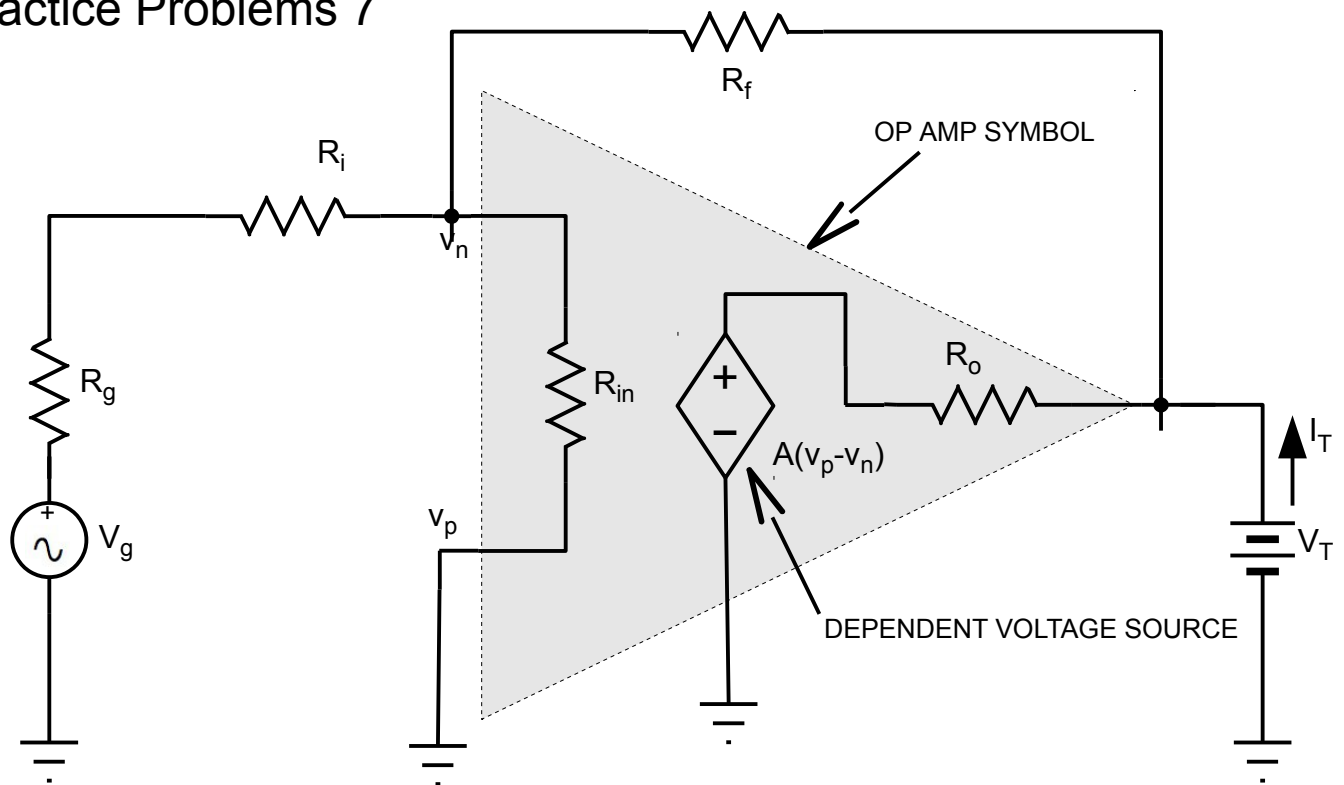

How does one compute the output impedance of an inverting op amp circuit (as opposed to the op amp itself)? One method is to use a slightly-more-realistic equivalent circuit (inside the dashed line of the op amp symbol), and then determine its Thévenin resistance. One can do this by applying Method B. The Thévenin resistance is the output impedance. Assume that  $R_g=0$ ,  $R_i=10\text{ K}\Omega$ ,  $R_f=10\text{ K}\Omega$ ,  $R_o=10\text{ }\Omega$ ,  $R_{in}=1\text{ M}\Omega$ , and  $A=1e5$ , and compute the output impedance of the op amp circuit. **You will see that the output resistance of the whole circuit is dramatically lower than that of the op amp itself.**

WARNING: the summing point constraints do not apply to the equivalent circuit!

The equivalent circuit for finding the output impedance  $R_{out}$  is shown. It consists of a test voltage source  $V_T$  in series with a resistor  $R_o$  and a dependent voltage source  $A(v_p - v_n)$ . The output current  $I_T$  is the current flowing out of the test source. The input side of the circuit is connected to node  $v_n$ , which is connected to ground through  $R_i$  and  $R_g$  (grouped as  $R_s$ ), and to the output node through  $R_f$ . The output node is also connected to ground through  $R_o$  and the dependent source.

Dependent voltage source:  $V_{ds} = A(v_p - v_n) = -Av_n$

①  $-I_T + \frac{V_T - (-Av_n)}{R_o} + \frac{V_T - v_n}{R_f} = 0$

Let  $R_s = R_i + R_g$

Then  $v_n = V_T \left( \frac{R_s \parallel R_{in}}{R_s \parallel R_{in} + R_f} \right) = V_T \left( \frac{R_s \cdot R_{in}}{R_s \cdot R_{in} + R_f(R_s + R_{in})} \right)$

Let  $K = \left( \frac{R_s \cdot R_{in}}{R_s \cdot R_{in} + R_f(R_s + R_{in})} \right)$

Then  $v_n = V_T K$

Plug into ①:

$-I_T + \frac{V_T + AV_T K}{R_o} + \frac{V_T(1-K)}{R_f} = 0$

$V_T \left( \frac{1}{R_o} + \frac{AK}{R_o} + \frac{1-K}{R_f} \right) = I_T$


$R_{out} = R_{th} = \frac{V_T}{I_T} = \frac{1}{\frac{1}{R_o} + \frac{AK}{R_o} + \frac{1-K}{R_f}} = 0.201e-3\Omega \ll R_o = 10\text{ }\Omega$

ECE3 Fall 2021  
Practice Problems 7

5

Find  $V_o = f(I_S, R)$ .

$$V_o = -I R$$

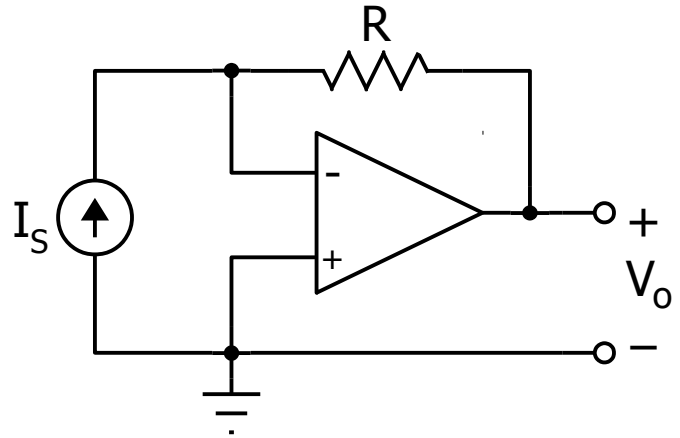

$$\text{By KCL, } \frac{v_n - V_o}{R} - I = 0$$

$$\text{But } v_n = 0$$

$$\therefore V_o = -IR$$

This is a *transimpedance amplifier*. Check it out.